

**Ryerson University**  
**Department of Electrical and Computer Engineering**  
**COE 328 – Digital Systems and Microprocessors**

**Midterm Test**

**October 27, 2008**

**Name:** \_\_\_\_\_ **Student Number:** \_\_\_\_\_ **Section:** \_\_\_\_\_

Time limit: 1 hour 50 min

Examiners: R. Sedaghat, N. Mekhiel

**Notes:**

- a) Closed book.
  - b) No calculators.
  - c) Answer all questions **in the space provided**.
  - d) Circle your professor's name and hand in these sheets.
- 

1. Implement function  $F = \overline{(x_1 \oplus x_3)} x_2 + (x_1 \oplus x_3) x_2$  using minimum number of multiplexers. Use 4-to-1 and 2-to-1 multiplexer. The inputs can be connected to either 1 or 0, or to any logic signal. **(8 marks)**

Name: \_\_\_\_\_

Section: \_\_\_\_\_

---

**2.** **(10 marks)**

**a)** Implement the following logic function using NAND gates only (Do not simplify)

$$F(x_1, x_2, x_3, x_4) = \sum m(0, 2, 5, 7, 8, 10)$$

Name: \_\_\_\_\_

Section: \_\_\_\_\_

---

**b)** Simplify the above function


**c)** Find the complement of the optimized function using DeMorgan theorem

Name: \_\_\_\_\_

Section: \_\_\_\_\_

3. a) Find the logic equation for the function  $f$  implemented in CMOS. Its PMOS circuit is shown below.

**(8 marks)**

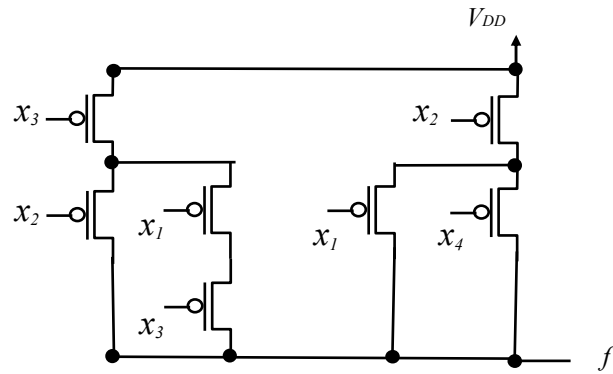

Name: \_\_\_\_\_

Section: \_\_\_\_\_

---

**b)** Simplify the above function

**c)** Implement the optimized function using CMOS

Name: \_\_\_\_\_

Section: \_\_\_\_\_

4. Given the binary 8 bit number 11101001, find the following: (8 marks)


a) The decimal value if the 8 bit number is an unsigned-number

b) The decimal value if the 8 bit number is signed-magnitude

c) The decimal value if the 8 bit number is 2's complement

d) Convert the 8 bit number to a hexadecimal-number

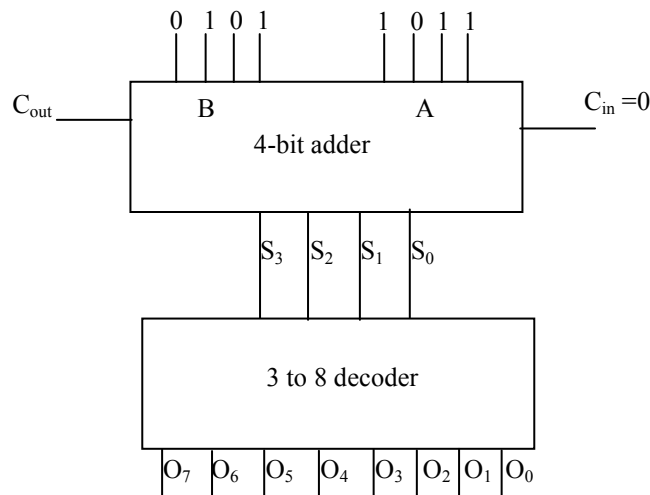5. Find the values of the outputs ( $O_7 \dots O_0$ ) for the circuit given below assuming  $A=1011$  and  $B=0101$  (5 marks)



Name: \_\_\_\_\_

Section: \_\_\_\_\_

---

6. Construct one -bit adder for two bits X and Y to generate a sum bit S and a Carry bit C using 2-to-1 multiplexers. **(5 marks)**

7. Show how the function  $f = x_3 \bar{x}_2 + x_1 x_2 + \bar{x}_3 x_2$  can be realized using the following circuit. Derive and write all values for the circuit inputs. The inputs can be connected to either 1 or 0, or to any logic signal. **(6 marks)**

