 


## Combinational Circuits 1-Multiplexers


Multiple inputs and only one selected by a select signal. The output = selected input

- 2 to 1 MUX and 4 to 1 MUX



 
## Multiplexer Expansion


- use 2 to 1 to build 4 to 1  
use 4 to 1 to build 16 to 1 MUX


 
## Multiplexer Applications Crossbar switch



 If  $s=0$  then  $Y_1=X_2$ ,  $Y_2=X_1$   
If  $s=1$  then  $Y_1=X_1$ ,  $Y_2=X_2$



## Synthesis of logic functions

1-Example:  $f = \sum 2, 3$

### Shanon's Expansion

$$f(w_1, w_2, \dots, w_n) = !w_1.f(0, w_2, \dots, w_n) + w_1.f(1, w_2, \dots, w_n)$$

$$\text{Example: } f = !w_1.w_2.w_3 + w_1.!w_2.w_3 + w_1.w_2.!w_3 + w_1.w_2.w_3$$

$$f = !w_3(w_1.w_2) + w_3.(!w_1.w_2 + w_1.!w_2 + w_1.w_2)$$

Example: using 2 to 1 MUX to implement

$$f = !w_1.!w_3 + w_1.w_2 + w_1.w_3$$

$$f = !w_3.!w_2.f(0, 0) + !w_3.w_2.f(0, 1) + w_3.!w_2.f(1, 0) + w_3.w_2.f(1, 1)$$


$$f = !w_3.!w_2.(!w_1) + !w_3.w_2.(!w_1 + w_1) + w_3.!w_2.(w_1) + w_3.w_2.(w_1 + w_1)$$

$$f = !w_1.(!w_3.!w_2 + !w_3.w_2) + w_1.(!w_3.w_2 + w_3.!w_2 + w_3.w_2)$$



$$f = !w_1.!w_3 + w_1.(w_3 + w_2)$$

©N. Mekhiel

## Shanon's expansion examples

 


$f = \text{sum of } m_2, m_3$

  

## Function Implementation using LUT


Example:  $f = !w1.!w3 + w1.w3 + w1.w2$

 
 
## Decoders


$n$  inputs generate  $2^n$  outputs, with only one = true based on value of  $n$

For 2 inputs , we have 4 outputs  
if input = 10, the output  $y_2=1$


 
## Decoder Expansion

Design 16 output decoder using 4 output decoders




## DeMultiplexer

Multiple outputs from single input selected by select line.

Could use a decoder, with  $En=i$

 Example: if  $i = 1$ ,  $s1 s0=10$ , then  $y2=1$



## **Encoders**

from n inputs, one is active and the output is the code for the specific input

Example: Binary encoder

4 inputs w3, w2, w1, w0

output is y1, y0

If  $w_3w_2w_1w_0=1000$ , then  $y_1y_0=11$

If  $w_3w_2w_1w_0=0100$ , then  $y_1y_0=10$

If  $w_3w_2w_1w_0=0010$ , then  $y_1y_0=01$

If  $w_3w_2w_1w_0=0001$ , then  $y_1y_0=00$

## **Priority Encoder**

If  $w_3w_2w_1w_0=1xxx$ , then  $y_1y_0=11$

If  $w_3w_2w_1w_0=01xx$ , then  $y_1y_0=10$

If  $w_3w_2w_1w_0=001x$ , then  $y_1y_0=01$

If  $w_3w_2w_1w_0=0001$ , then  $y_1y_0=00$

$$y_0 = w_3 + w_1 \cdot !w_2 \cdot !w_3$$

$$y_2 = w_3 + !w_3 \cdot w_2$$


©N. Mekhiel

## Code Conversion

From BCD to 7 Segment Display

segment a= 0+2+3+5+6+7+8+9

 Use a 4 to 16 decoder , then OR gate for each segment



©N. Mekhiel

## **Arithmetic Comparator**

If  $A = a_3a_2a_1a_0$ , and  $B = b_3b_2b_1b_0$  then:

$$A \text{eq } B = !(a_3 \text{ XOR } b_3) \cdot !(a_2 \text{ XOR } b_2) \cdot \\ !(a_1 \text{ XOR } b_1) \cdot !(a_0 \text{ XOR } b_1)$$

$$A \text{gt } B = a_3 \cdot !b_3 + !(a_3 \text{ XOR } b_3) \cdot a_2 \cdot !b_2 \\ + !(a_3 \text{ XOR } b_3) \cdot !(a_2 \text{ XOR } b_2) \cdot a_1 \cdot !b_1 \\ + !(a_3 \text{ XOR } b_3) \cdot \\ !(a_2 \text{ XOR } b_2) \cdot !(a_1 \text{ XOR } b_1) \cdot a_0 \cdot !b_0$$

$$A \text{lt } B = !(A \text{eq } B + A \text{gt } B)$$

©N. Mekhiel

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY mux4to1 IS
PORT( w0, w1, w2, w3: IN STD_LOGIC;
      s       : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
      f       : OUT STD_LOGIC);
END mux4to1;

ARCHITECTURE Behavior OF mux4to1 IS
BEGIN
  WITH s SELECT
    f<= w0 WHEN "00",
              w1 WHEN "01",
              w2 WHEN "10",
              w3 WHEN OTHERS;
END Behavior;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY dec2to4 IS
    PORT( w      : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          En     : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
          y      : OUT STD_LOGIC_VECTOR(3 DOWNTO 0));
END dec2to4;

ARCHITECTURE Behavior OF dec2to4 IS
    SIGNAL Enw : STD_LOGIC_VECTOR (2 DOWNTO 0);
BEGIN
    Enw <= En & w;
    WITH Enw SELECT
        y<= "1000" WHEN "100",
                    "0100" WHEN "101",
                    "0010" WHEN "110",
                    "0001" WHEN "111"
                    "0000" WHEN OTHERS;
END Behavior;
```

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY encod IS
    PORT( w      : IN STD_LOGIC_VECTOR(3 DOWNTO 0);
          y      : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
          z      : OUT STD_LOGIC);
END encod;

ARCHITECTURE Behavior OF encod IS
BEGIN
    PROCESS(w)
    BEGIN
        IF w(3) = '1' THEN
            y <="11";
        ELSEIF w(2) = '1' THEN
            y<= "10";
        ELSEIF w(1) = '1' THEN
            y<= "01";
        ELSE
            y<= "00";
        END IF;
    END PROCESS;
    z<= '0' WHEN w = "0000" ELSE "1";
END Behavior;
```

## Ch6

6.2 Use 3 to 8 decoder and an OR gate to implement:

$$f = \sum m_1, m_2, m_3, m_5, m_6$$

Decoder inputs X<sub>1</sub>, X<sub>2</sub>, X<sub>3</sub> and outputs y<sub>0..y7</sub>

$$f = y_1 + y_2 + y_3 + y_5 + y_6$$

6.3 use 2 to 1 MUX to implement :

$$f = !w_1.!w_3 + w_2.!w_3 + !w_1.w_2$$

w<sub>1</sub> w<sub>2</sub> w<sub>3</sub> f

0 0 0 1

0 0 1 0

0 1 0 1

0 1 1 1

-----

1 0 0 0

1 0 1 0

1 1 0 1

1 1 1 0

$$f = !w_1.(!w_2.!w_3 + w_2.!w_3 + w_2.w_3) + w_1.(w_2.!w_3)$$

$$f = !w_1.(!w_3 + w_2) + w_1.(w_2.!w_3)$$

©N. Mekhiel

6.11 use minimum of 2 inputs LUTs to implement:

$$f = !w_1 \cdot !w_2 + !w_2 \cdot !w_3 + w_1 \cdot w_2 \cdot w_3$$

using Shanon expansion in w2

$$f = !w_2 \cdot (!w_1 + !w_3) + w_2 \cdot (w_1 \cdot w_3)$$

assume g=w1.w3 then !g= !w1+!w3

$$f = g \cdot w_2 + !g \cdot !w_2$$

6-16 show how to implement :

$$f = w_2 \cdot !w_3 + w_1 \cdot w_3 + !w_2 \cdot w_3$$

use Shanon

$$\begin{aligned} f &= !w_3 \cdot (w_2) + w_3 \cdot (w_1 + !w_2) = !w_3 \cdot (w_2) \\ &+ w_3 \cdot (w_1 \cdot w_2 + !w_2) \end{aligned}$$

6-18- given VHDL Code find the circuit

y0=1 if w =00, En=1

y2=1 if w=10 and En=1

This is a 2 to Decoder

©N. Mekhiel