

2008  
2009

Ryerson University  
 Department of Electrical and Computer Engineering  
 COE 328 – Digital Systems and Microprocessors

Midterm Test

October 27, 2008

Name: \_\_\_\_\_

Student Number: \_\_\_\_\_

Section: \_\_\_\_\_

Time limit: 1 hour 50 min

Examiners: N. Mekhiel, R. Sedaghat

Notes:


- Closed book.
- No calculators.
- Answer all questions in the space provided.
- Circle your professor's name and hand in these sheets.

- minimum number of  
 1. Implement function  $F = (\overline{x_1} \oplus x_2) \overline{x_3} + (x_1 \oplus x_2) x_3$  using multiplexers. (?? marks)

3 input XOR truth table

$x_1$	$x_2$	$x_3$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$F = x_1 \oplus x_2 \oplus x_3$$

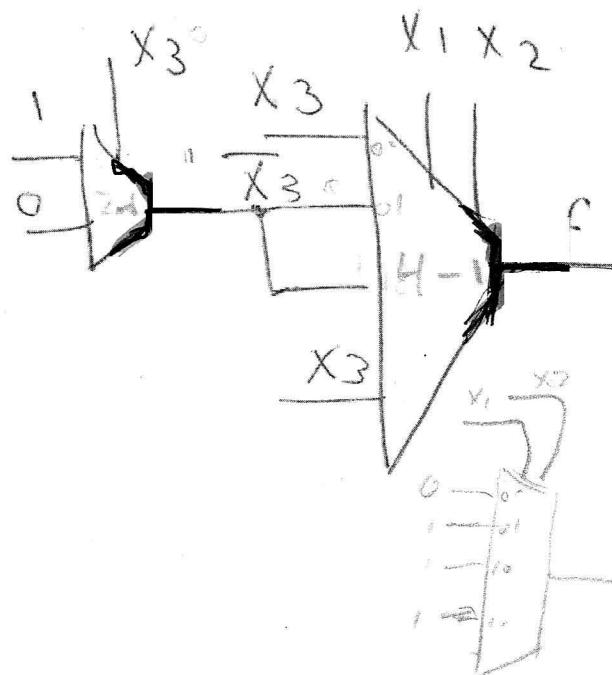


$$\begin{aligned} \overline{x} \overline{y} + \overline{x} y &= \\ &= \overline{x} \oplus y \end{aligned}$$

2.

(?? marks)

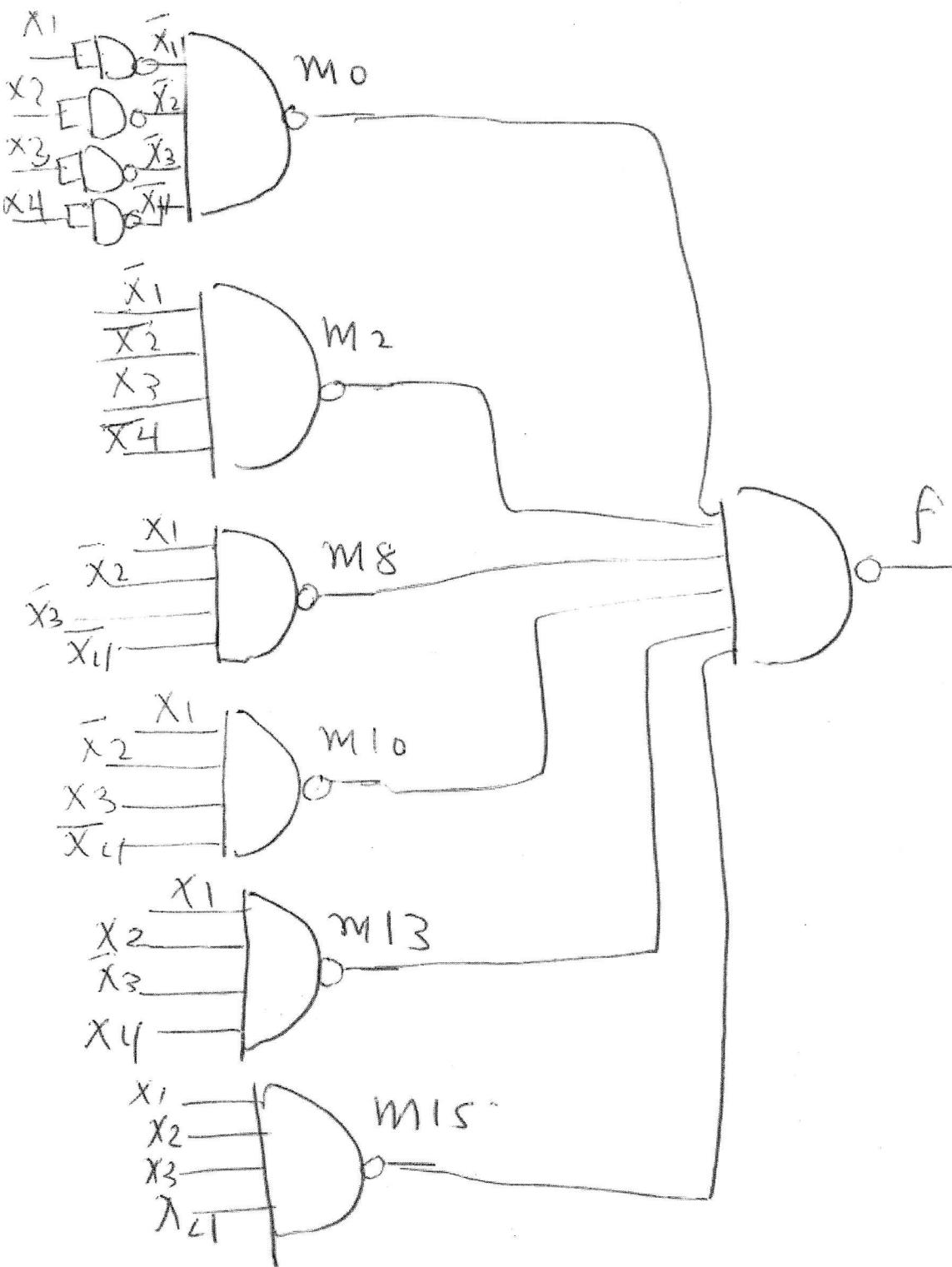a) Implement the following logic function using NAND gates only (Do not simplify)


$$F(x_1, x_2, x_3, x_4) = \sum m(0, 2, 8, 10, 13, 15)$$



Name: \_\_\_\_\_

### Section:

b) Simplify the above function

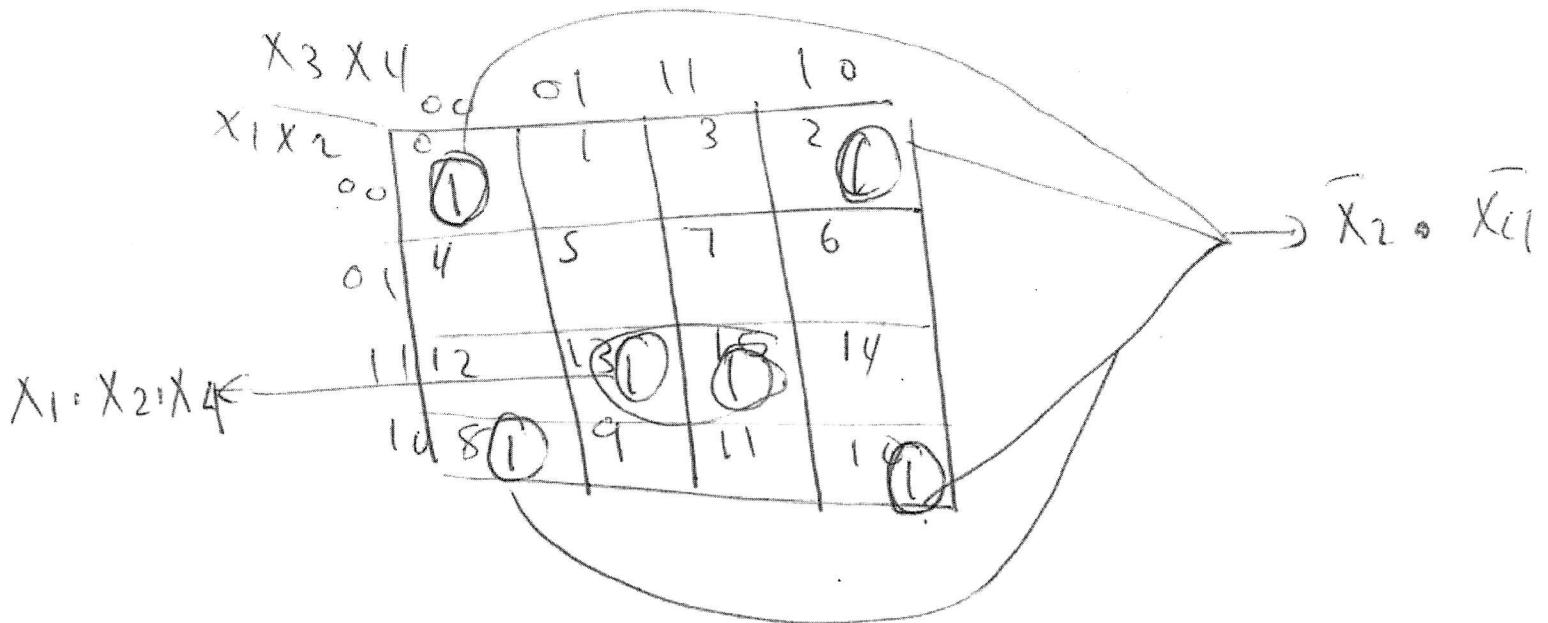

$$f = x_1 \cdot x_2 \cdot x_4 + \overline{x_2} \cdot \overline{x_4}$$

c) Find the complement of the optimized function using DeMorgan theorem


$$\bar{F} = (\bar{x}_1, \bar{x}_2, \bar{x}_3 + \bar{x}_4)$$

$$= (\bar{x}_1 + \bar{x}_2 + \bar{x}_4) \circ (x_2 + x_4)$$

$$= \bar{x}_1 \cdot x_2 + \bar{x}_1 \cdot x_4 + \bar{x}_2 \cdot x_4 + \bar{x}_4 \cdot x_2$$

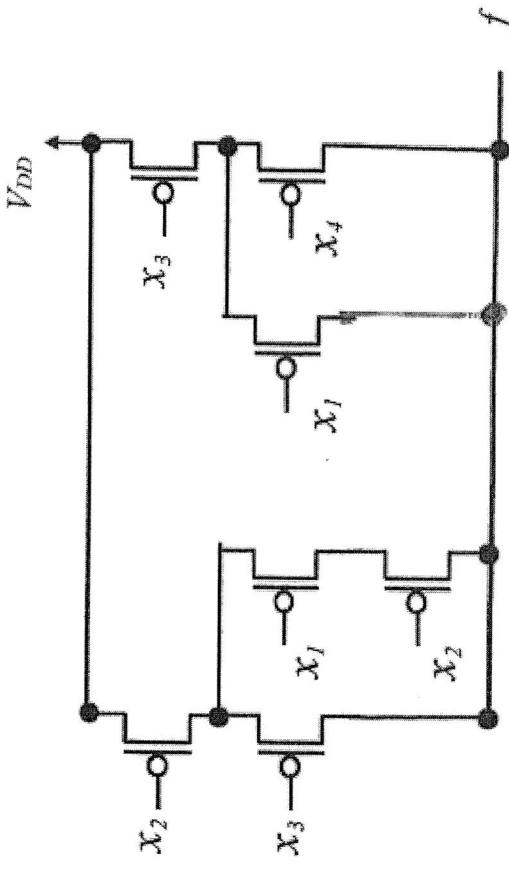3. a) Find the logic equation for the function  $f$  implemented in CMOS. Its PMOS circuit is shown below.  
(?? marks)

~~$P(x_1 \cdot \overline{x}_2 \cdot \overline{x}_3 + x_2 \cdot \overline{x}_3 \cdot \overline{x}_1)$~~



$$F = \overline{x}_2 \cdot (\overline{x}_3 + \overline{x}_1 \cdot \overline{x}_2) + \overline{x}_3 \cdot (\overline{x}_1 + \overline{x}_4)$$

Name: \_\_\_\_\_


Section: \_\_\_\_\_

b) Simplify the above function


$$F = \bar{x}_2 \cdot \bar{x}_3 + \bar{x}_1 \cdot \bar{x}_2 + \bar{x}_3 \cdot \bar{x}_4 + \bar{x}_3 \cdot \bar{x}_4$$

$$= \bar{x}_3 (\bar{x}_2 + \bar{x}_1 + \bar{x}_4) + \bar{x}_1 \cdot \bar{x}_2$$

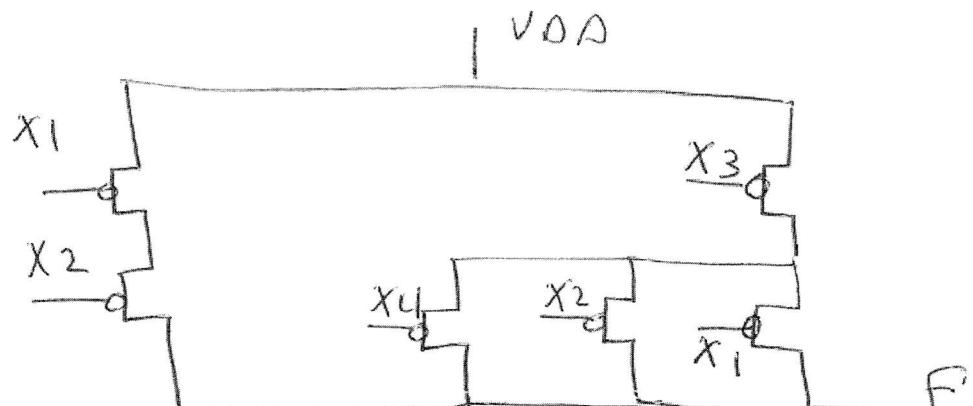c) Implement the optimized function using CMOS


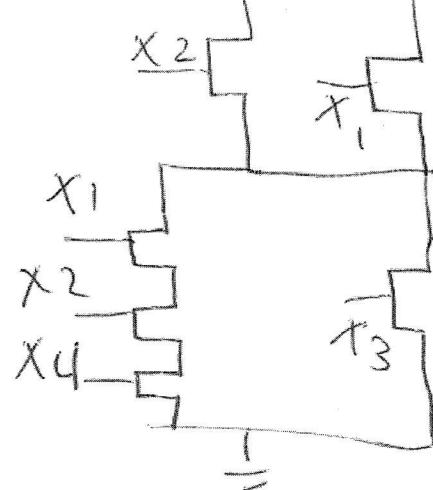
$$\bar{F} = (x_1 + x_2) \cdot (x_3 + x_1 \cdot x_2 \cdot x_4)$$



Name: \_\_\_\_\_

Section: \_\_\_\_\_

4. Given the binary 8 bit number 11011001, find the following:

- a) The decimal value if the 8 bit number is an unsigned-number

$$\cancel{(1+8+16+64)} + 128 = 25 + 64 + 128 = 217$$

- b) The decimal value if the 8 bit number is signed-magnitude

$$-(1+8+16+64) = -89$$


- c) The decimal value if the 8 bit number is 2's complement

$$-(0100111) = -(1+2+4+32) = -39$$

- d) Convert the 8 bit number to a hexadecimal-number

D9	Dec	9	10	11	12	13	14	15	16
	Hex	A	B	C	D	E	F	10	

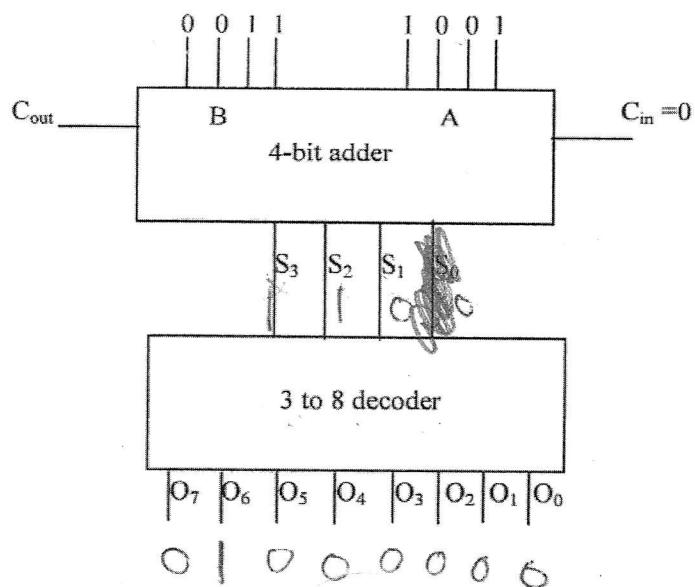5. Find the values of the outputs ( $O_7 \dots O_0$ ) for the circuit given below assuming A=1001 and B=0011



$$S = \begin{array}{r} 1001 \\ 0011 \\ \hline 1100 \end{array}$$

Name: \_\_\_\_\_

Section: \_\_\_\_\_

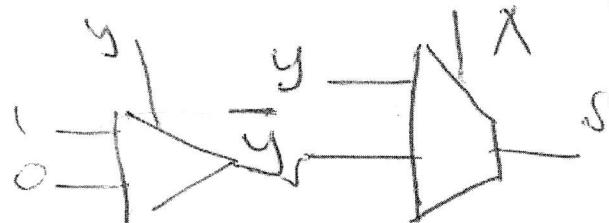
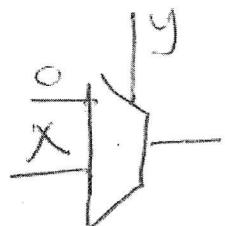
6. Construct a one-bit adder using a 2-to-1 multiplexer



(?? marks)




$$\text{S} = \cancel{\text{X} \cdot \text{Y} + \bar{\text{X}} \cdot \bar{\text{Y}}} = \text{X} \cdot \bar{\text{Y}} + \bar{\text{X}} \cdot \text{Y}$$



7. Show how the function  $f = x_2 \bar{x}_3 + x_1 x_3 + \bar{x}_2 x_3$  can be realized using the following circuit. Derive and write all values for the circuit inputs.

(?? marks)

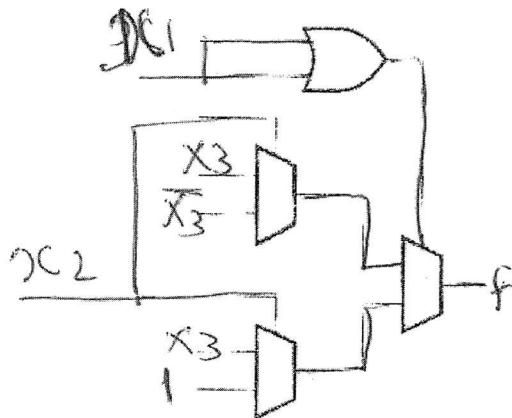

$$\begin{aligned} f &= \bar{x}_1 \cdot \bar{x}_2 (x_3) + \bar{x}_1 \cdot M_2 (\bar{x}_3) \\ &\quad + x_1 \cdot \bar{x}_2 (x_3) + x_1 \cdot x_2 (\bar{x}_3 + x_3) \end{aligned}$$