

ELE328: DIGITAL SYSTEMS AND MICROPROCESSORS

- Introduction
 - Scope and Objectives
 - Course Management
- Introduction to Logic Circuits
 - Variables and Functions

© N. Mekhiel

Scope and Objectives

- Design of Basic Digital Logic Circuits, and Implementation in Appropriate Technology
- Digital Circuits include Combinational and Sequential Circuits from simple circuits to microprocessor
- Use CAD Tools for design entry (Schematics, VHDL), verification using simulation and implementation in appropriate technology

© N. Mekhiel

Course Management

course information:

<http://www.ee.ryerson.ca/~courses/ele328>

- Instructor: Nagi Mekhiel Ext 7251
Email: nmekhiel@ee.yerson.ca
- Text Book:
 - Fundamentals of Digital Logic with VHDL Design, Brown and Varensic, 1st edition, McGraw-Hill
 - Introduction To Digital Logic Design, Hayes, Addison Wesley
 - Any VHDL Reference
 - ELE328 Lab Manual

© N. Mekhiel

Logic Circuits

- **Logic Variables and Functions**

- Binary variable X has two values: TRUE OR FALSE

$X = 1$ (TRUE) , $X = 0$ (FALSE)

Variable representation: SWITCH

SWITCH ON variable = TRUE(=1)

SWITCH OFF variable = FALSE(0)


- Logic Function :

Example $F(X) = X$

If input variable $X=0$,

Output Function $F(X)=X=0$

Implementation: Use SWITCHES

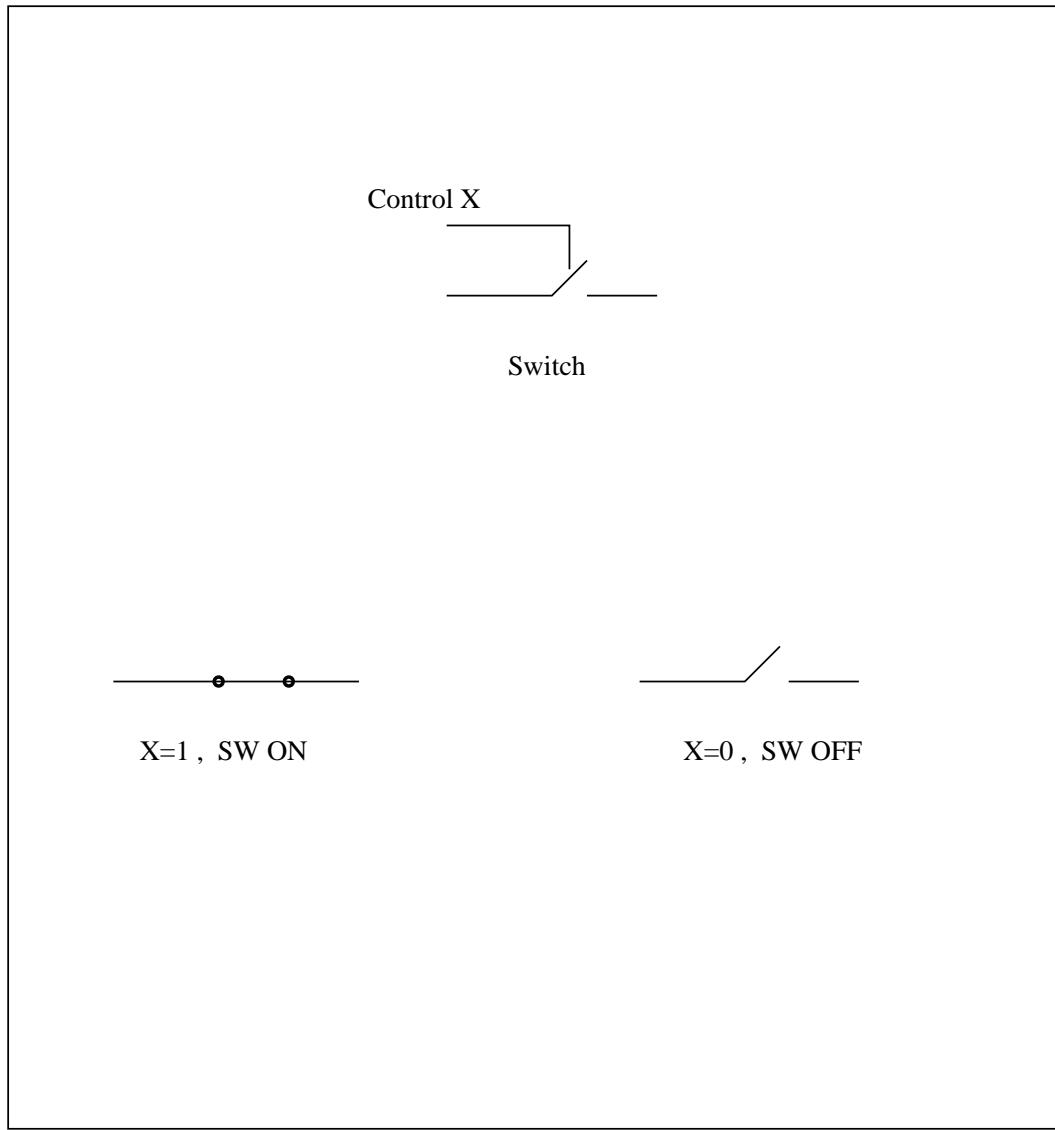

F(X)=X Function Implementation

© N. Mekhiel

Different Logic Functions

AND Logic Function :


$$F(X_1, X_2) = X_1 \cdot X_2$$

Behavior : OUTPUT is TRUE IF X_1 AND X_2 are TRUE

Example: Find $X_1 \cdot X_2$ if $X_1=1$, $X_2=1$

$$X_1 \text{ AND } X_2 = X_1 \cdot X_2 = 1 \cdot 1 = 1$$

Symbol and Implementation

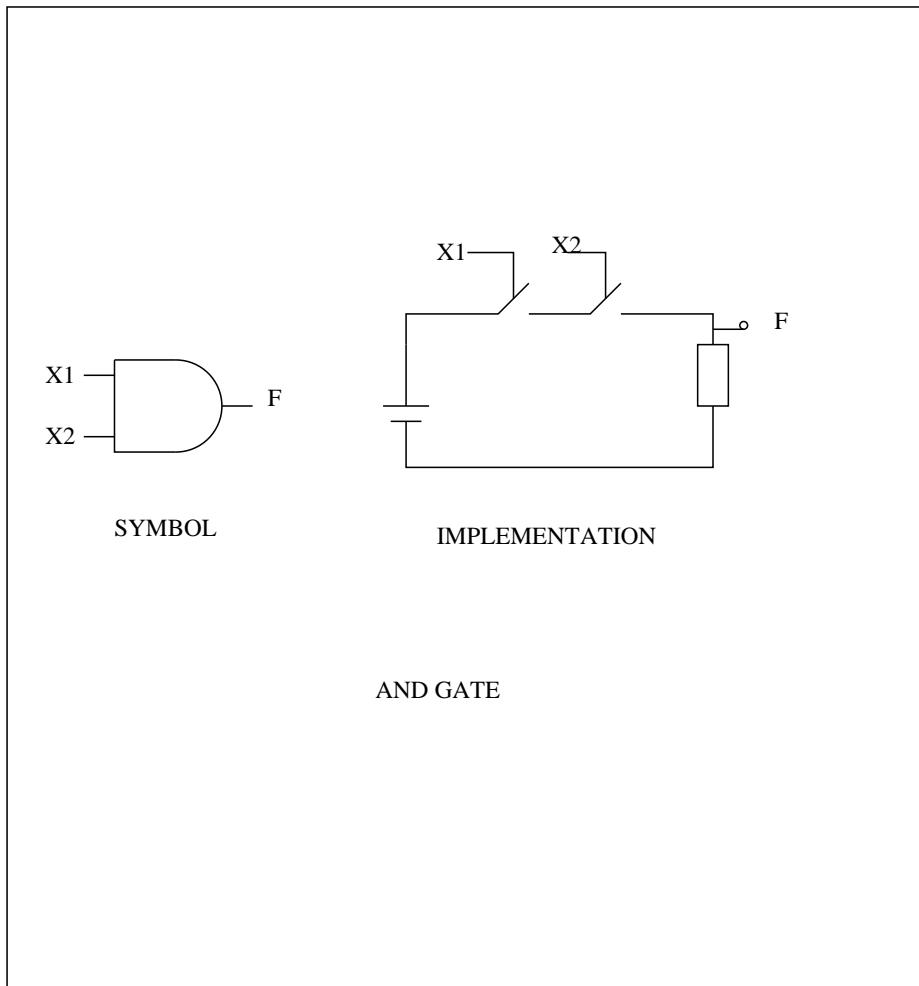

Different Logic Functions

OR Logic Function :


$$F(X_1, X_2) = X_1 + X_2$$

Behavior : OUTPUT is TRUE IF X_1 OR X_2 IS TRUE

Example: Find $X_1 + X_2$ if $X_1=1$, $X_2=1$

$$X_1 \text{ OR } X_2 = X_1 + X_2 = 1 + 1 = 1$$

Symbol and Implementation

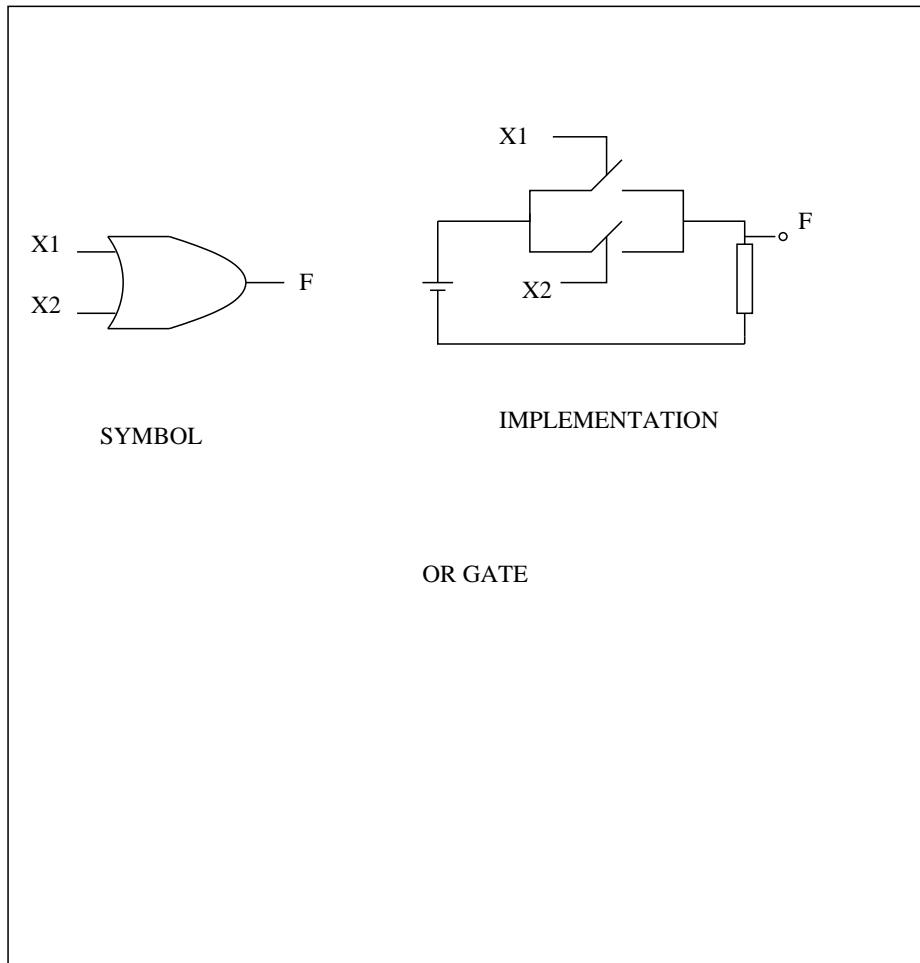

Different Logic Functions


INV Logic Function : $F(X_1) = !X_1$

Behavior : OUTPUT is TRUE IF X_1 IS FALSE

Example: Find $!X_1$ if $X_1=1$

$$!X_1 = 0$$

Symbol and Implementation

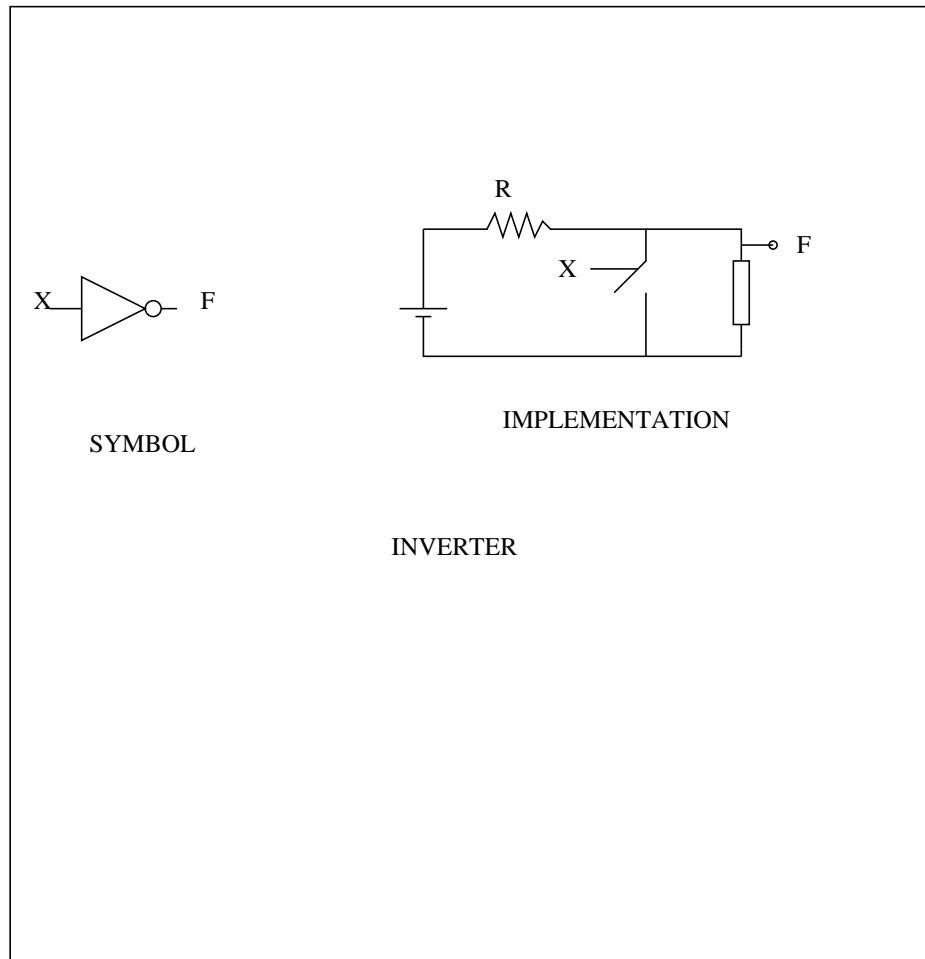

The Truth Table

- Representation of complicated Logic Functions
- Gives all information to design logic function
- Table of outputs for all possible input conditions
- For three inputs (X_1, X_2, X_3), Conditions = $2^3 = 8$


©N. Mekhiel

X1	X2	X3	Out
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

© N. Mekhiel

Logic Gates

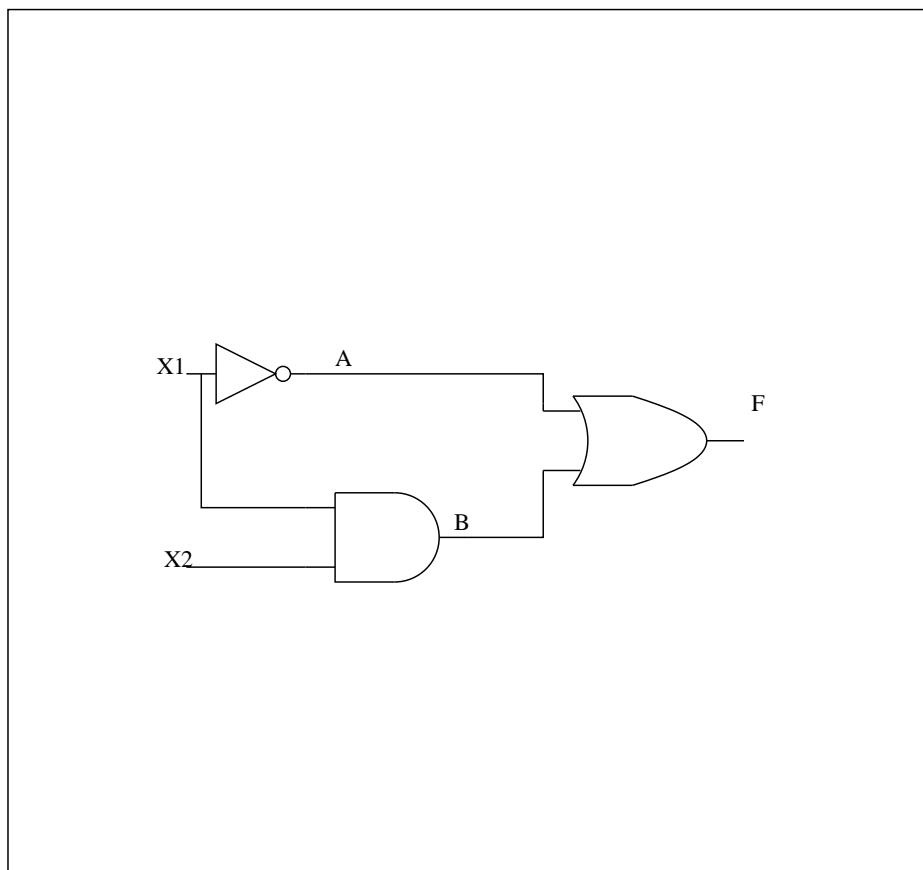- **Analysis of Logic Gates:**
 - Find Logic Function from Schematic
 - Find Truth Table from Logic Function
 - Find Timing Diagram to Verify Function
- Example: Given the Schematic below



- Logic Function of the Schematic
 $A = \neg X_1$, $B = X_1 \cdot X_2$
 $F(X_1, X_2) = A + B = \neg X_1 + X_1 \cdot X_2$
- Truth Table of the Logic Circuit above


X1	X2	F
0	0	1
0	1	1
1	0	0
1	1	1

- Timing Diagram:

©N. Mekhiel

Functionally Equivalent Circuits

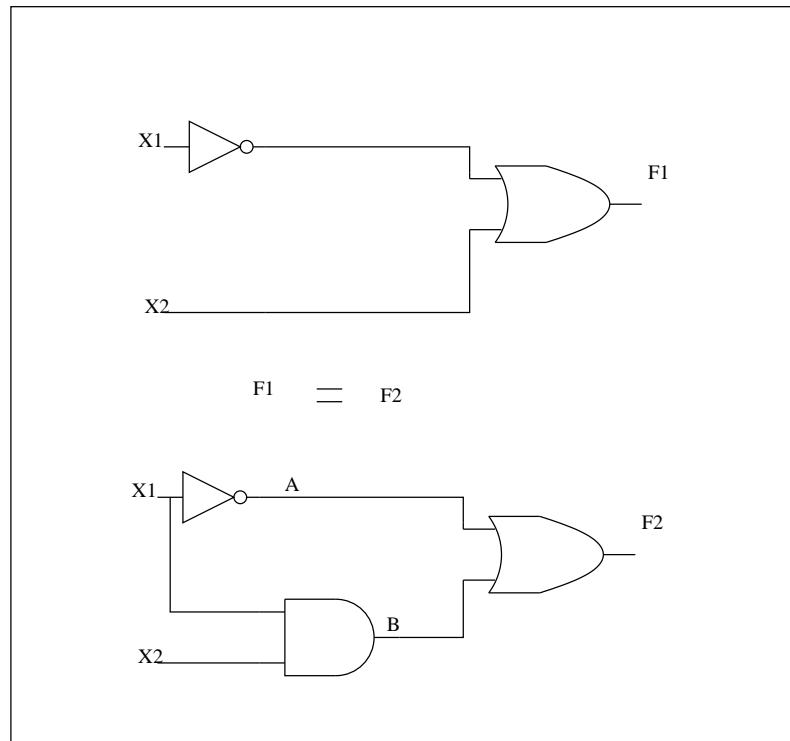- Logic Functions could be implemented using different Circuits
- Example: Consider the Circuit Below:



Functionally Equivalent Circuits

- $F1 = !X1 + X2$
- Truth Table of the Logic Circuit above

X1	X2	F1=F2
0	0	1
0	1	1
1	0	0
1	1	1

© N. Mekhiel

- Boolean Algebraic Rules:
- Used for Optimization of Logic Functions
 - $X \cdot 0 = 0$, $X \cdot 1 = X$
 - $X + 1 = 1$, $X + 0 = X$
 - $X \cdot X = X$, $X + X = X$
 - $X \cdot !X = 0$, $X + !X = 1$
 - $!(!X) = X$
 - $X \cdot Y = Y \cdot X$, $X + Y = Y + X$ (Could optimize wire Routing)
 - $X \cdot (Y \cdot Z) = (X \cdot Y) \cdot Z$, $X + (Y + Z) = (X + Y) + Z$
 - $X \cdot (Y + Z) = X \cdot Y + X \cdot Z$
 - Prove that: $(X + Y) \cdot (X + Z) = X + YZ$

$$\begin{aligned} LHS &= X \cdot X + X \cdot Z + Y \cdot X + Y \cdot Z \\ &= X(1 + Y + Z) + YZ = X + YZ \end{aligned}$$

- Prove that $X+X.Y=X$
 $LHS=X.(1+Y)=X.1$
- **DeMorgan's Theorem**
 - $!(X+Y) = !X.Y$
 - $!(X.Y) = !X + !Y$
 - Useful to implement Functions using different gates
 - Example: Find $!(X_1.X_2 + (Y_1+!X_2))$


$$= !(X_1.X_2). !(Y_1+!X_2)$$

$$= (!X_1+!X_2).(!Y_1.X_2)$$

$$= !X_1.Y_1.X_2 + !X_2.Y_1.X_2 = !X_1.Y_1.X_2$$

©N. Mekhiel

Venn Diagram

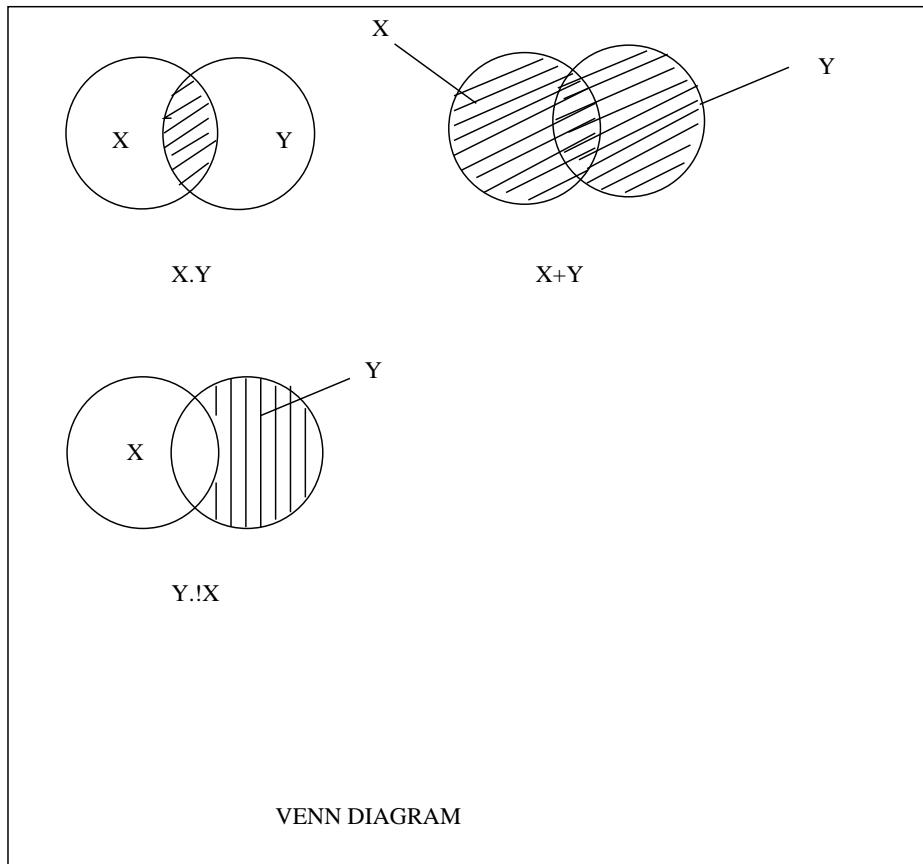

Graphical representation of logic operations
©N. Mekhiel

Synthesis of Logic Functions (Implementation)

- **Method1: Sum of Products**

- Construct a Truth Table
- Find each condition where the output=1, call this a minterm
- Use AND function to implement each minterm so that the output=1, this is a product term
- Take the SUM of all product terms using OR function

©N. Mekhiel

- Use the sum of product to implement the following:

cond	X1	X2	F	product term
0	0	0	1	$m_0 = \bar{X}_1 \cdot \bar{X}_2$
1	0	1	1	$m_1 = \bar{X}_1 \cdot X_2$
2	1	0	0	
3	1	1	1	$m_3 = X_1 \cdot X_2$

Logic Function= Sum of Products


$$F = m_0 + m_1 + m_3$$

$$F = \bar{X}_1 \cdot \bar{X}_2 + \bar{X}_1 \cdot X_2 + X_1 \cdot X_2$$

©N. Mekhiel

Circuit Implementation: Using AND - OR
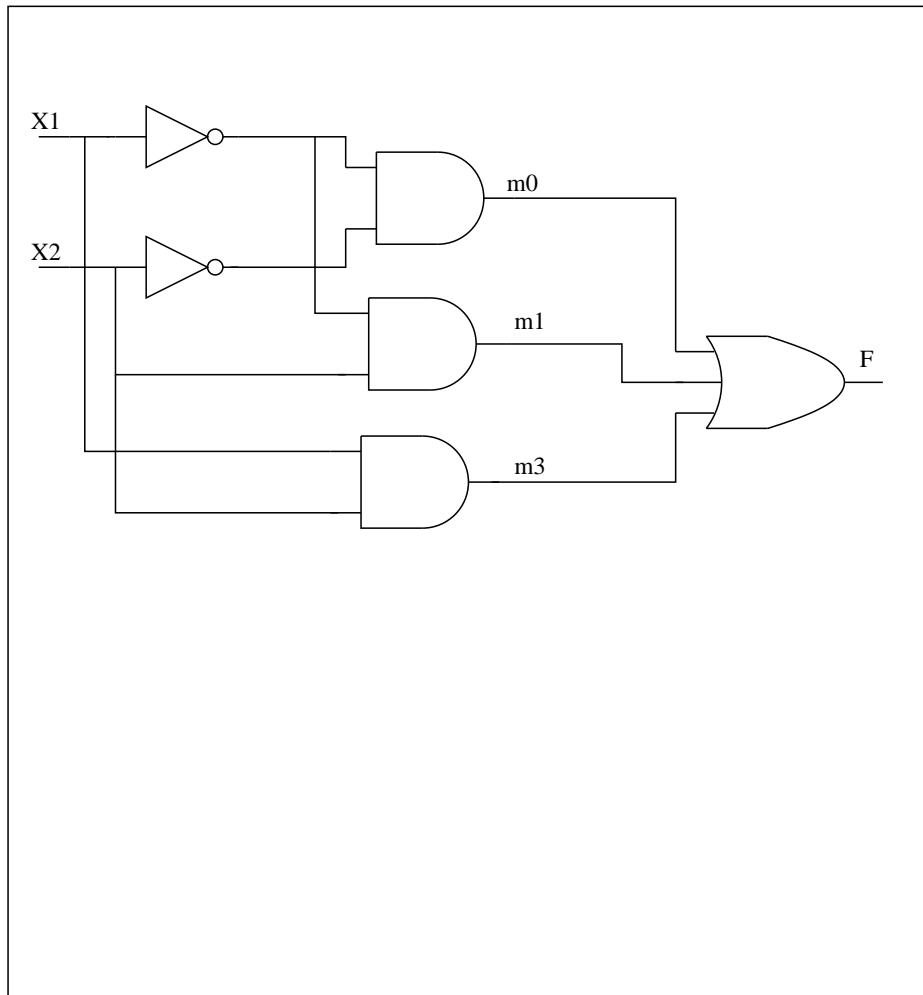
$$F = \overline{X_1} \cdot \overline{X_2} + \overline{X_1} \cdot X_2 + X_1 \cdot X_2$$



©N. Mekhiel

- **Method2: Product Of Sums**

- Construct a Truth Table
- Find each condition where the output=0, call this a Maxterm
- Use OR function to implement each Maxterm
so that the output=0, this is a sum term
- Take the PRODUCT of all SUM terms using AND function

©N. Mekhiel

- Use the product of sums to implement the following:


cond	X1	X2	F	MAX term
0	0	0	0	$M_0 = X_1 + X_2$
1	0	1	1	
2	1	0	0	$M_2 = !X_1 + X_2$
3	1	1	1	

- Logic Function= Product of SUMS
- $F = M_0 \cdot M_2 = (X_1 + X_2) \cdot (!X_1 + X_2)$

©N. Mekhiel

$$F = M_0 \cdot M_2 = (X_1 + X_2) \cdot (\bar{X}_1 + \bar{X}_2)$$

Circuit Implementation using OR - AND

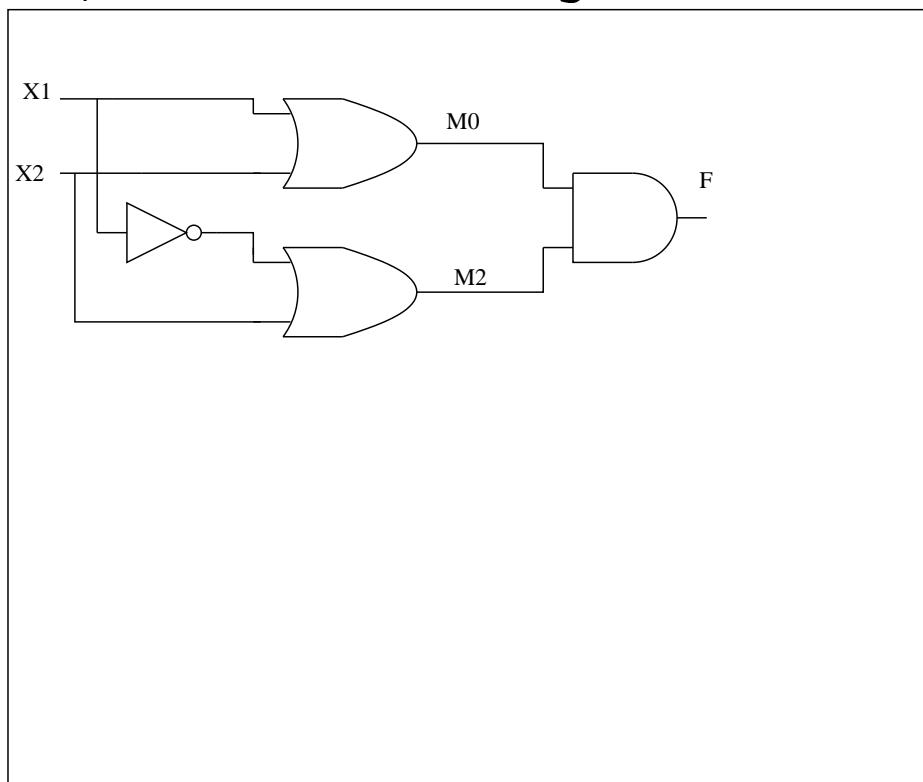

©N. Mekhiel

- Example: Design a Majority function for three inputs such that output=1 if two or more inputs=1

X1	X2	X3	Out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

©N. Mekhiel

Using Sum Of Products and Product of Sums

- Using sum of products $F = m_3 + m_5 + m_6 + m_7$
 $F = !X_1 \cdot X_2 \cdot X_3 + X_1 \cdot !X_2 \cdot X_3$
 $+ X_1 \cdot X_2 \cdot !X_3 + X_1 \cdot X_2 \cdot X_3$
- Using product of sums $F = M_0 \cdot M_1 \cdot M_2 \cdot M_4$
 $F = (X_1 + X_2 + X_3) \cdot (X_1 + X_2 + !X_3)$
 $\cdot (X_1 + !X_2 + X_3) \cdot (!X_1 + X_2 + X_3)$

©N. Mekhiel

Introduction to CAD Tools

Computer Aided Design Software to automatically Design, Verify and Implement complex systems

Design Steps:

- Design Entry:
 - Using **Schematic Diagram**, enter symbol of each gate and connect gates to get the design (takes time, could have mistakes, easy to understand and follow design)
 - Using **Truth Table from waveforms**, only for combinational circuits, might not cover all conditions)
 - Using **VHDL** Hardware Description Language, easy to change, faster design, better documentation and is portable (does not depend on type of gates)


©N. Mekhiel

Introduction to CAD Tools

Computer Aided Design Software to automatically Design, Verify and Implement complex systems

Design Steps:

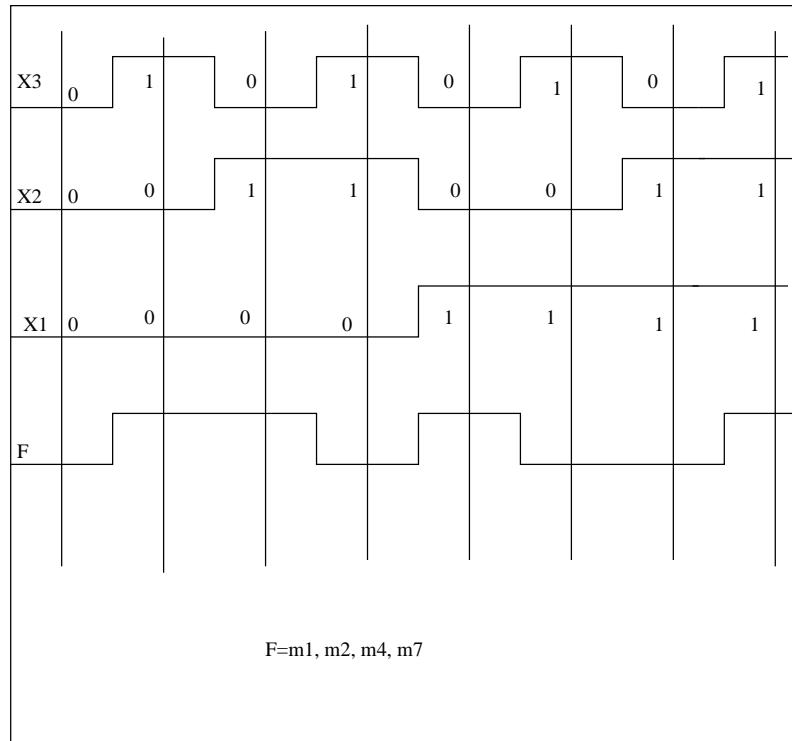- Functional Simulation: use different input conditions in form of waveforms to verify the design (test vectors)



- Synthesis: Generate a logic circuit from design according to target technology

Introduction to VHDL

Consists of:

- Declaration: to define inputs and outputs


```
ENTITY Funct IS
    PORT(X1,X2,X3 : IN STD_LOGIC;
          F         : OUT STD_LOGIC);
END Funct;
```

- Architecture to describe the circuit behavior

```
ARCHITECTURE LogicFunction OF Funct IS
BEGIN
    F<=(X1ANDX2)OR(NOTX2ANDX3);
END LogicFunction;
```

©N. Mekhiel

CAD System

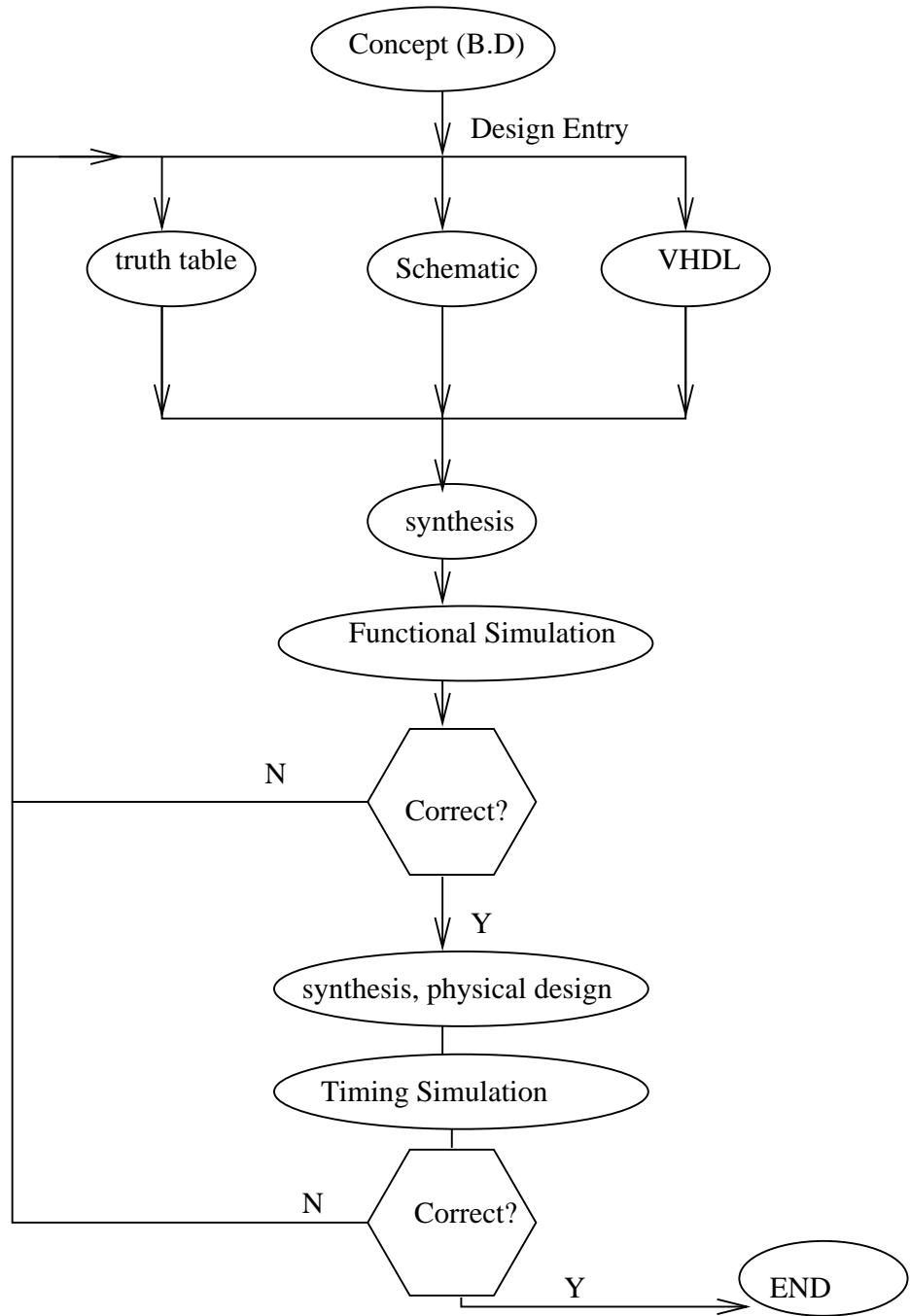

Solutions to Selected Problems

1-Prove that:

$$\begin{aligned} & !X_1 \cdot X_3 + X_1 \cdot X_2 \cdot !X_3 + !X_1 \cdot X_2 + X_1 \cdot !X_2 = \\ & !X_2 \cdot X_3 + X_1 \cdot !X_3 + X_2 \cdot !X_3 + !X_1 \cdot X_2 \cdot X_3 \end{aligned}$$

Solution: Expand L.H.S and R.H.S. to standard minterms using the boolean algebraic rule: $A = A \cdot (X_1 + !X_1)$

$$\begin{aligned} \text{R.H.S} &= !X_1 \cdot X_3 (X_2 + !X_2) + X_1 \cdot X_2 \cdot (X_3 + !X_3) \\ &\quad + X_1 \cdot !X_2 (X_3 + !X_3) \\ &= m_1, m_2, m_3, m_4, m_5, m_6 = \text{L.H.S} \end{aligned}$$

2- Show that sum of $m_1, m_2, m_3, m_4, m_5, m_6, m_7$
 $= X_1 + X_2 + X_3$

$$m_1, m_3 = !X_1 \cdot !X_2 \cdot X_3 + !X_1 \cdot X_2 \cdot X_3 = !X_1 \cdot X_3$$

$$m_5, m_7 = X_1 \cdot !X_2 \cdot X_3 + X_1 \cdot X_2 \cdot X_3 = X_1 \cdot X_3$$

$$\text{Combine } m_1, m_3, m_5, m_7 = !X_1 \cdot X_3 + X_1 \cdot X_3 = X_3$$

$$m_4, m_5, m_6, m_7 \text{ gives } X_1$$

$$m_2, m_3, m_6, m_7 \text{ gives } X_2$$

Solutions to Selected Problems

3-Design Simplest circuit for $f(X_1, X_2, X_3)$
= SUM of 1,3,4,6,7

Solution:

$$1,3 = \bar{X}_1 \cdot \bar{X}_2 \cdot X_3 + \bar{X}_1 \cdot X_2 \cdot X_3 = \bar{X}_1 \cdot X_3$$

$$4,6 = X_1 \cdot \bar{X}_2 \cdot \bar{X}_3 + X_1 \cdot X_2 \cdot \bar{X}_3 = X_1 \cdot \bar{X}_3$$

$$3,7 = \bar{X}_1 \cdot X_2 \cdot X_3 + X_1 \cdot X_2 \cdot X_3 = X_2 \cdot X_3$$

$$F = \bar{X}_1 \cdot X_3 + X_1 \cdot \bar{X}_3 + X_2 \cdot X_3$$

4-Design Simplest circuit for $f(X_1, X_2, X_3)$
= Product of 0,1,5,7

Solution:

use the following rule $(A+X_1) \cdot (A+\bar{X}_1) = A$

$$0,1 = (X_1+X_2+X_3) \cdot (X_1+X_2+\bar{X}_3) = (X_1+X_2)$$

$$5,7 = (\bar{X}_1+X_2+\bar{X}_3) \cdot (\bar{X}_1+X_2+\bar{X}_3) = (\bar{X}_1+\bar{X}_3)$$

$$F = (X_1+X_2) \cdot (\bar{X}_1+\bar{X}_3)$$