RYERSON UNIVERSITY

Department of Electrical and Computer Engineering

ELE 635 Communication Systems

Phase Locked Loop and Carrier Recovery


Winter 2015

Overview

In this week's lectures we will discuss **two topics** that are fundamental in the design of many communication systems.

These topics are:

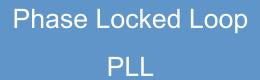- Phase Locked Loop (PLL).
- Carrier Recovery/Acquisition.




What is a Phase Locked Loop (PLL)?


The PLL is a control system that is used to track the (potentially) time-varying phase and the instantaneous frequency of the carrier component of a signal.

It is an extremely useful system that allow synchronous (coherent) demodulation of modulated signals. It is also a fundamental component in the demodulation of angle modulated (PM and FM) signals.


PLLs are also used in the frequency synthesis and detection of FSK-formatted digital signals.

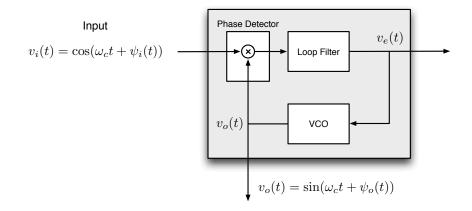

ELE 635 - Winter 2015 RYERSON UNIVERSITY

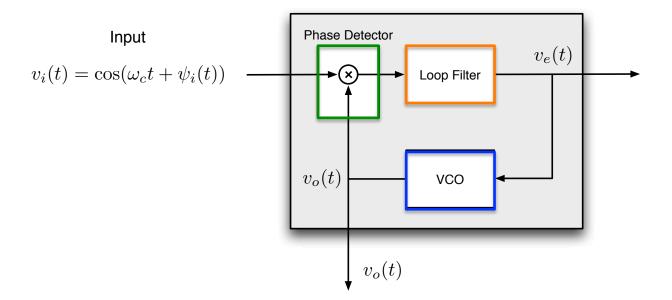

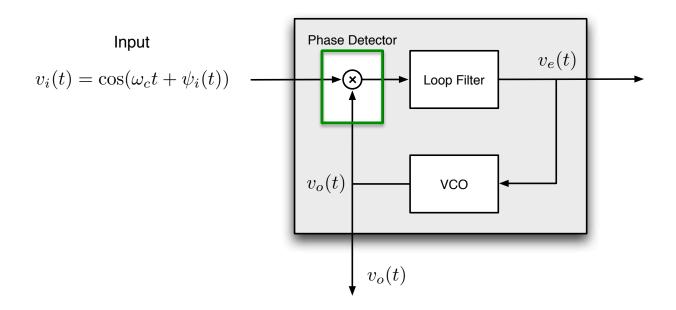
- **Phase Detector**
- **Loop Filter**
- Voltage controlled oscillator **VCO**




Phase Detector

PD acts as a multiplier, to be more precise the PD includes a multiplier, a filter and an amplitude scaling unit. For our initial discussion it is sufficient to consider the PD unit as a multiplier only.

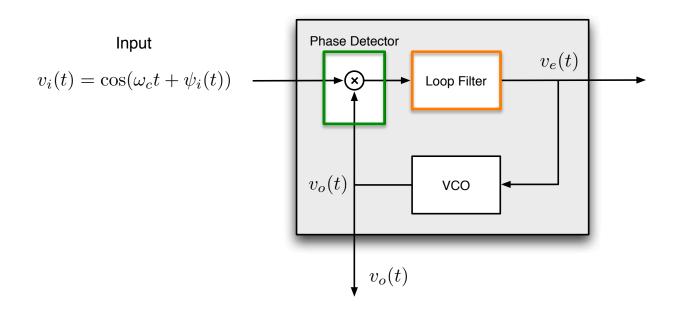RYERSON UNIVERSITY ELE 635 – Winter 2015 6




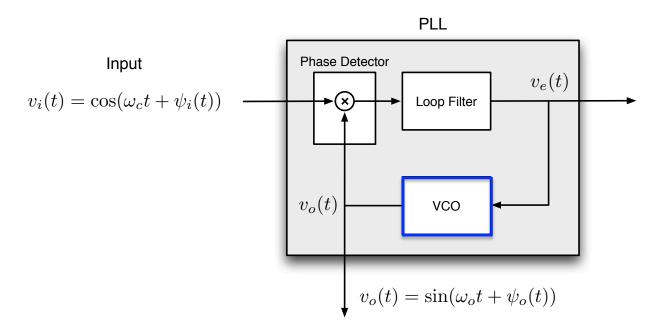
- **Phase Detector**
- Loop Filter The loop filter is a narrowband lowpass filter.



- Phase Detector
- Loop Filter
- Voltage controlled oscillator (**VCO**) an oscillator whose output can be controlled by the voltage level at its input $v_e(t)$

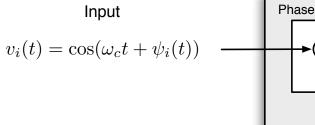
RYERSON UNIVERSITY ELE 635 – Winter 2015 8



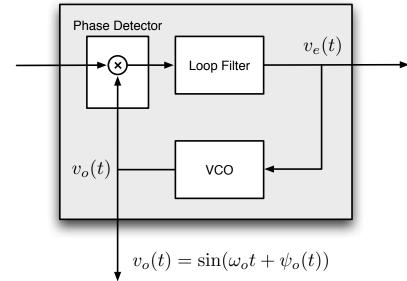


PLL

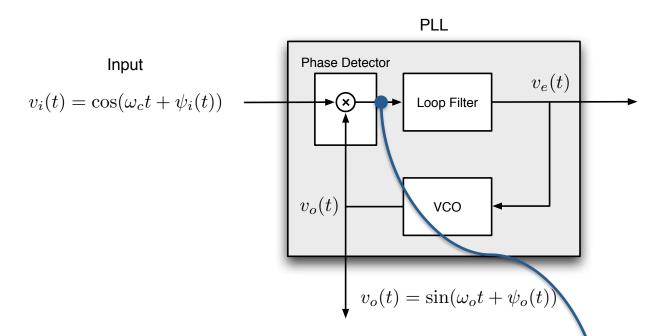- PLL functions as a closed loop feedback system.
- Objectives:
 - Lock the VCO frequency to that of the incoming signal
 - Track changes in the instantaneous frequency of v_i(t).





Phase detector output:
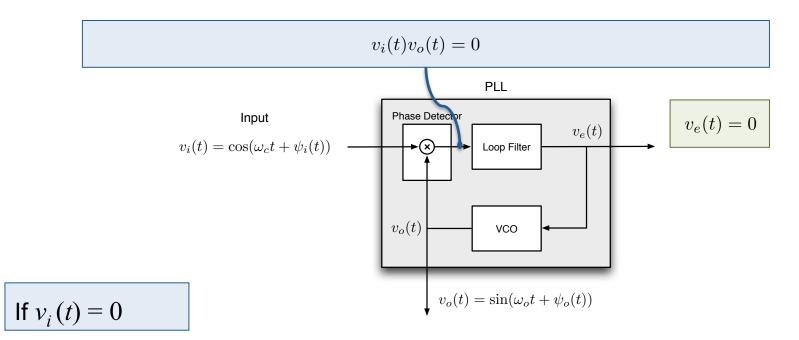
$$v_i(t)v_o(t) \sim \cos(\omega_c t + \psi_i)\sin(\omega_o t + \psi_o)$$
$$\sim \sin((\omega_c - \omega_o)t + (\psi_i - \psi_o)) + \sin((\omega_c + \omega_o)t + (\psi_i + \psi_o))$$



 - $v_i(t)v_o(t) = 0$
- Loop filter output: $v_e(t) = 0$
- VCO continues to operate at its free running frequency f_{θ}



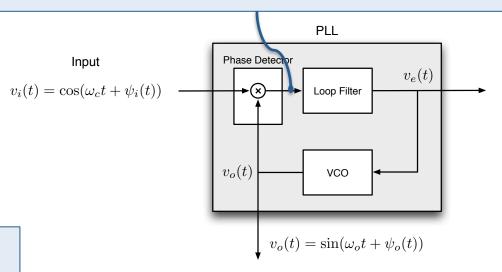

•
$$v_i(t)v_o(t) \neq 0$$

If $v_i(t) \neq 0$


• PD generates the signal $v_i(t)v_o(t)$ with frequency components at $f_c \pm f_0$

Which of the two frequency components at

$$f_c \pm f_0$$

will make it through the Loop Filter?



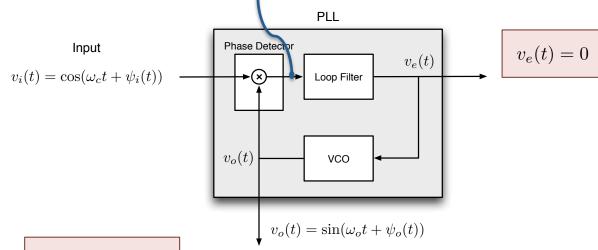



If
$$v_i(t) \neq 0$$
 and $|f_0 - f_c| > \gamma$

- Both frequency components in $v_i(t)v_o(t)$ will be eliminated by the loop filter.
- Loop filter output: $v_e(t) = 0$
- VCO continues to operate at its free running frequency.

Superheterodyne

Receivers

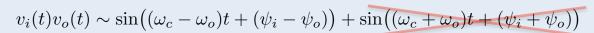


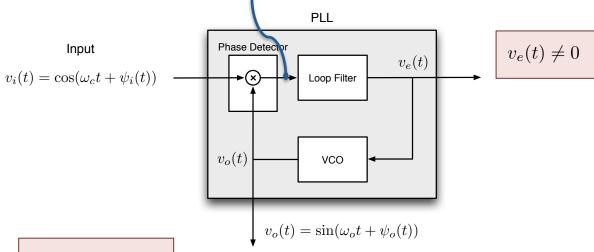

If $v_i(t) \neq 0$ and $|f_0 - f_c| < \gamma$

- Frequency component at $f_c + f_0$ will be eliminated by the loop filter.
- Frequency component at $f_c f_\theta$ will be within the passband of the loop filter.
- Loop filter output: $v_e(t) \neq 0$
- VCO will change its output ... How?
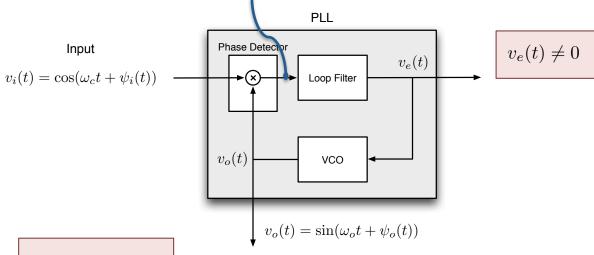
$$v_i(t)v_o(t) \sim \sin((\omega_c - \omega_o)t + (\psi_i - \psi_o)) + \sin((\omega_c + \omega_o)t + (\psi_i + \psi_o))$$



If
$$v_i(t) \neq 0$$
 and $|f_0 - f_c| < \gamma$

• $v_e(t) \neq 0$ VCO frequency changes to reduce the error signal.

• $|f_0 - f_c| < \gamma$ VCO will lock to the instantaneous frequency of $v_i(t)$


PLL will track the instantaneous frequency of $v_i(t)$

Given that


$$v_i(t) = \cos(2\pi f_c t + \psi_i(t))$$

Initial PLL set-up

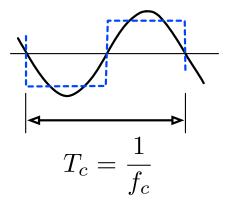- Set VCO frequency to equal to the carrier frequency $\longrightarrow f_0 = f_c$
- VCO output has 90° phase shift with respect to the unmodulated carrier:
 - o unmodulated carrier $\cos 2\pi f_c t$
 - o free-running VCO output $\implies \sin 2\pi f_0 t = \sin 2\pi f_c t$ such that PD output equals 0.
- The VCO waveform used in most PLLs is a square-wave.




A square wave is easier to generate

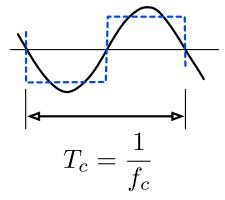


- A square wave is easier to generate
- Given the more accurate phase detector model:

PD = Multiply + Filter + Amplitude Scale

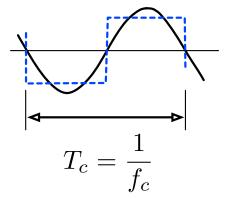

- A square wave is easier to generate
- Given the more accurate phase detector model:

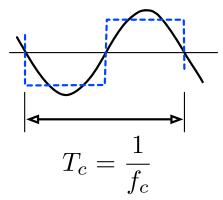
and the representation of a square wave as:





- A square wave is easier to generate
- Given the more accurate phase detector model:

and the representation of a square wave as:

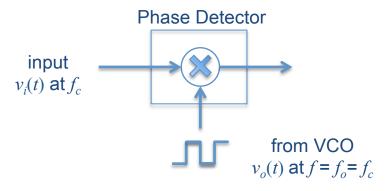after multiplication and filtering, the PD output will only include the fundamental term $\implies \sin 2\pi f_0 t$




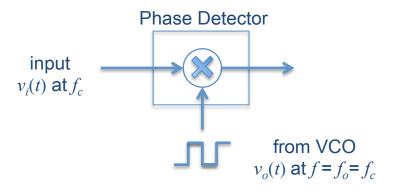


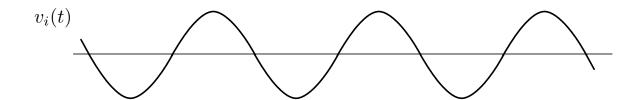


Superheterodyne

Receivers

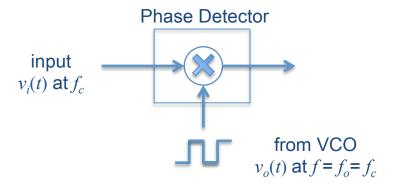


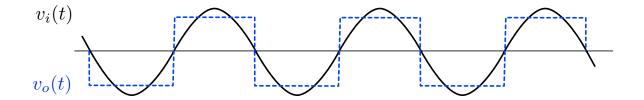


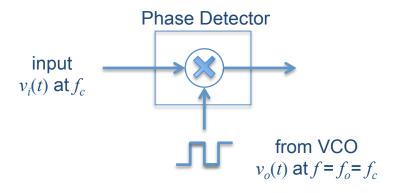

Case 1


 $v_i(t)v_o(t)$

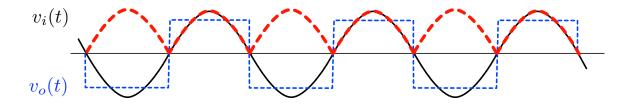


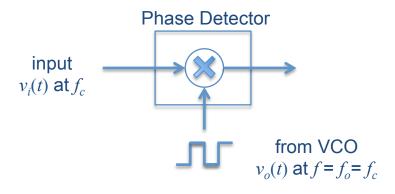


Case 1

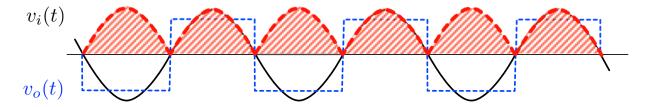
Phase Detector output $\sim \text{Area}[v_i(t)v_o(t)] =$ maximum



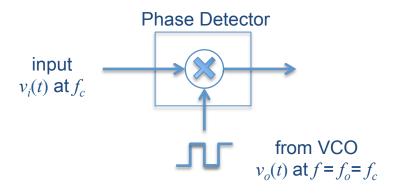


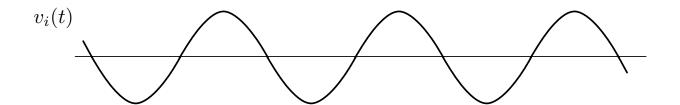
$$\begin{cases} v_i(t) = \cos 2\pi f_c t \\ v_o(t) = \sin 2\pi f_o t = \cos(2\pi f_c t - \pi/2) \end{cases} \qquad \psi_e = \psi_0(t) - \psi_i(t) = -\frac{\pi}{2}$$



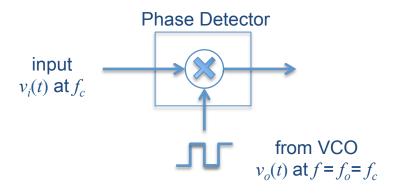

$$\begin{cases} v_i(t) = \cos 2\pi f_c t \\ v_o(t) = \sin 2\pi f_o t = \cos(2\pi f_c t - \pi/2) \end{cases} \qquad \psi_e = \psi_0(t) - \psi_i(t) = -\frac{\pi}{2}$$

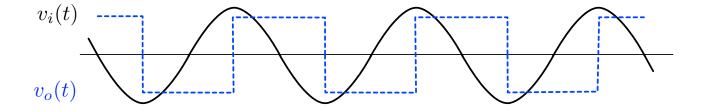


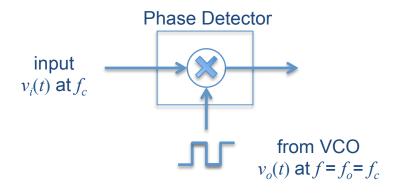


Case 2

$$\begin{cases}
v_i(t) = \cos 2\pi f_c t \\
v_o(t) = \sin 2\pi f_o t = \cos(2\pi f_c t - \pi/2)
\end{cases} \qquad \psi_e = \psi_0(t) - \psi_i(t) = -\frac{\pi}{2}$$

 $v_i(t)v_o(t)$

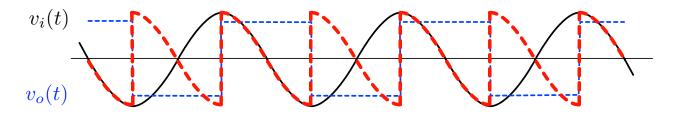


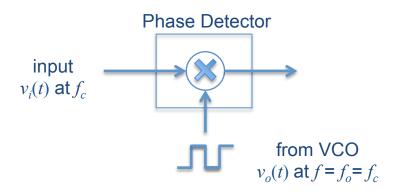


Case 2

$$\begin{cases} v_i(t) = \cos 2\pi f_c t \\ v_o(t) = \sin 2\pi f_o t = \cos(2\pi f_c t - \pi/2) \end{cases} \qquad \psi_e = \psi_0(t) - \psi_i(t) = -\frac{\pi}{2}$$

Phase Detector output $\sim \text{Area}[\ v_i(t)v_o(t)\]= 0$

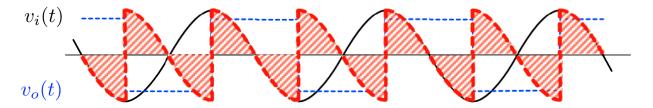

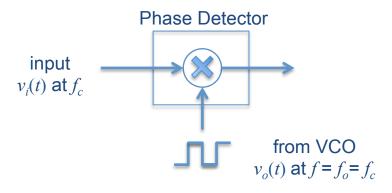


Case 3

$$v_i(t) = \cos 2\pi f_c t$$


$$v_o(t) = -\cos 2\pi f_o t = -\cos 2\pi f_c t$$

$$\phi_e = -\pi$$

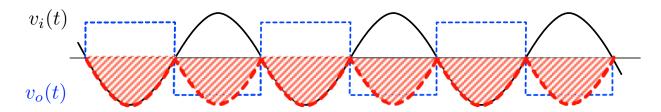Phase Detector output $\sim \text{Area}[v_i(t)v_o(t)] = \text{minimum}$



PLL: Operational parameters

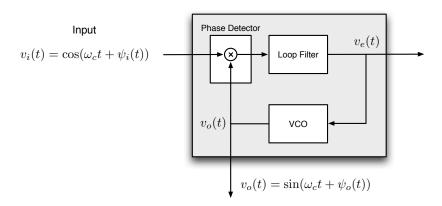

• f_{θ} Free-running / Centre frequency

frequency at which the VCO operates when not locked to the input signal, i.e., when $v_e(t) = 0$. Pre-set externally.

• f_L Lock / Tracking / Hold-in range


frequency range in the vicinity of f_{θ} over which the PLL once locked to the input will remain in lock.

• f_n Capture / Pull-in / Acquisition range

Maximum initial frequency difference between f_{θ} and f_{c} $|f_{\theta}-f_{c}|$ for which the PLL can acquire lock.

RYERSON UNIVERSITY ELE 635 – Winter 2015 31


How to measure?

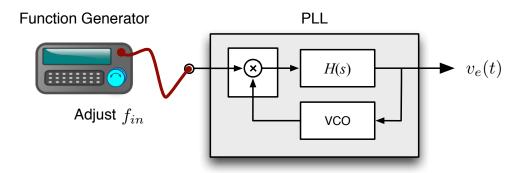

- Fix VCO free-running frequency at $f_0 = f_c$
- Change (increase


) input frequency f_{in}

• Measure $v_e(t)$

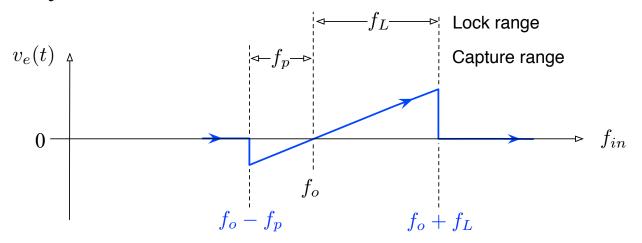


PLL: Operational parameters

How to measure?

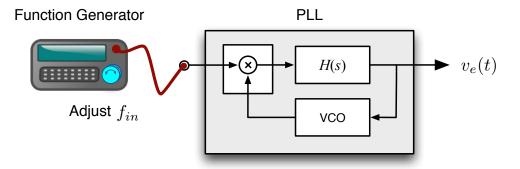


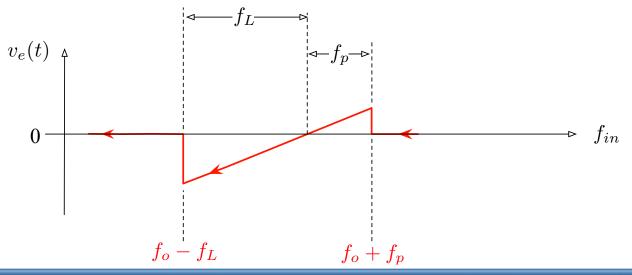- Fix VCO free-running frequency at $f_0 = f_c$
- Change ($\frac{\text{decrease}}{\text{decrease}}$) input frequency f_{in}
- Measure $v_e(t)$




PLL: Operational parameters

How to measure?

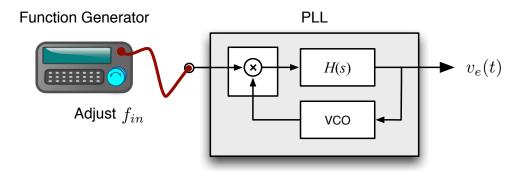

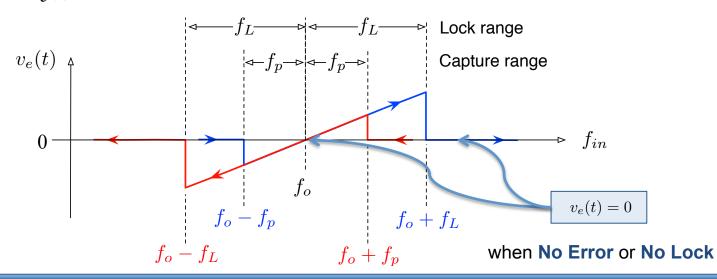
- Fix VCO free-running frequency at $f_0 = f_c$
- Change (increase and decrease) input frequency f_{in}
- Measure $v_e(t)$



Narrow bandwidth PLL: narrow-band tracking / bandpass filter

Coherent Demodulation: a modulated waveform with a separate carrier
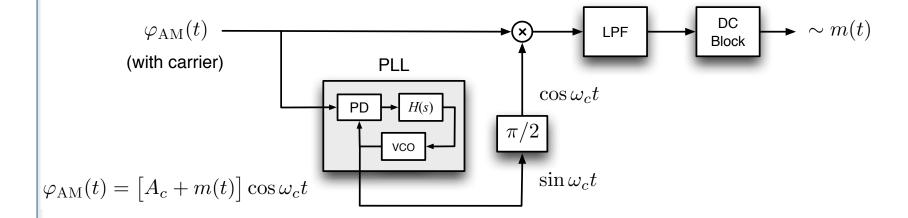
$$\varphi_{\rm AM}(t) = [A_c + m(t)] \cos \omega_c t$$




RYERSON UNIVERSITY ELE 635 – Winter 2015 35

Wide bandwidth PLL: FM demodulation


$$\varphi_{\mathrm{FM}}(t) = \cos(\omega_c t + K_f \int m(\lambda) d\lambda)$$

RYERSON UNIVERSITY ELE 635 – Winter 2015 36

Sweep Acquisition

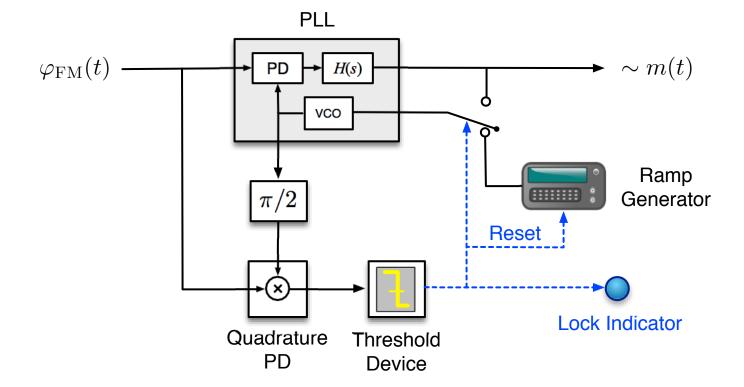

Frequency Synthesis

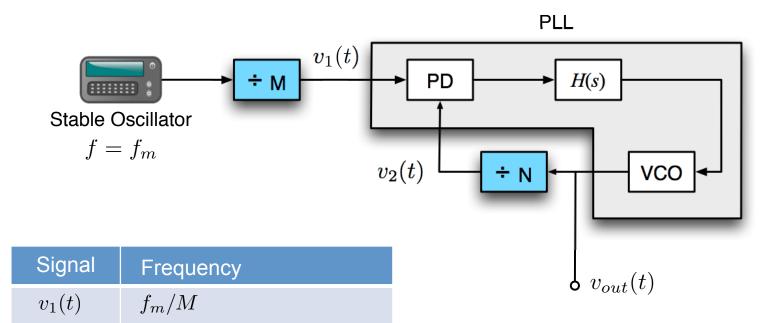


 $v_2(t)$


 $v_{out}(t)$


 $f_2 = f_{out}/N = f_m/M$

 $f_{out} = (N/M)f_m$

Coherent FSK Demodulation

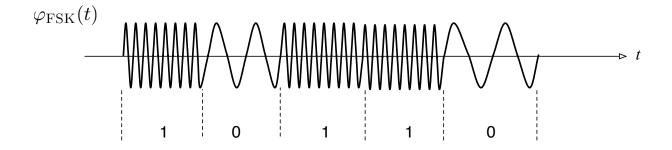

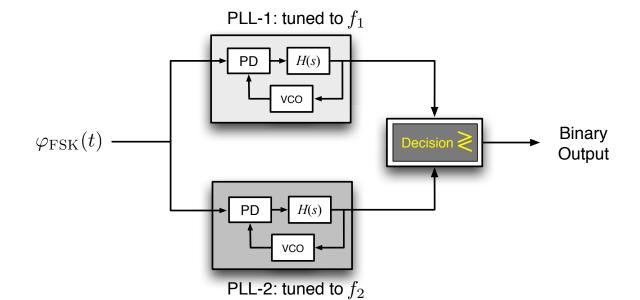

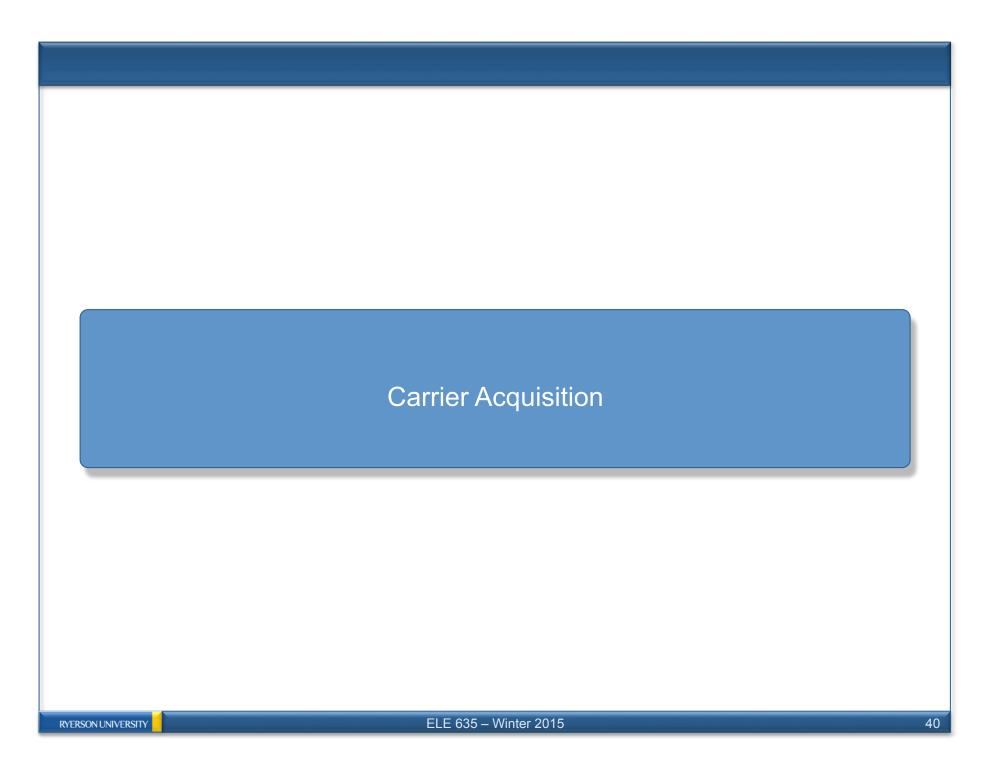

How to demodulate

Modulated signals with a carrier (DSB-LC, SSB+C, VSB+C ...)

non-coherent / envelope detection

or

coherent detection

How to demodulate

- Modulated signals with a carrier (DSB-LC, SSB+C, VSB+C ...)
 - non-coherent / envelope detection or coherent detection
- Suppressed carrier modulated signals (DSB-SC, SSB, VSB ...)

coherent detection

How to demodulate

Modulated signals with a carrier (DSB-LC, SSB+C, VSB+C ...)

non-coherent / envelope detection or coherent detection

Suppressed carrier modulated signals (DSB-SC, SSB, VSB ...)

coherent detection

- For coherent (or synchronous) detection we need to generate a local carrier at the receiver.
- Any discrepancy in the frequency or phase of the local carrier creates distortion in the detector output.

Carrier Acquisition is the process of generating a local carrier in the receiver that is frequency and phase synchronized with the carrier used in the transmitter.

Carrier Acquisition is the process of generating a local carrier in the receiver that is frequency and phase synchronized with the carrier used in the transmitter.

An alternative:


- Add a separate carrier/pilot to the modulated signal at a reduced level (typically 20 dB below the signal power).
- Converts suppressed carrier signal into a small carrier format.
- This may be the only viable solution to synchronize RX with TX.

Of course, at the RX we still need the signal processing components to lock onto and track the pilot tone.

Carrier Acquisition for Signals with a Carrier

PLL can be used to track both the frequency and the phase of the carrier.

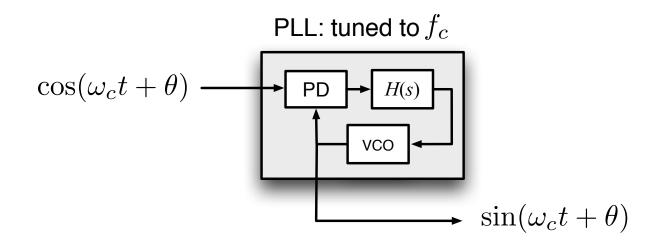- Used for coherent/synchronous demodulation of DSB-LC/AM signals
- Can also used in wide-band PLL mode for demodulating FM/PM signals.



A DSB-SC amplitude modulated waveform of the form

$$\varphi_{\text{DSB-SC}} = m(t)\cos\omega_c t$$

does not have a separate carrier term.

A DSB-SC amplitude modulated waveform of the form

$$\varphi_{\text{DSB-SC}} = m(t)\cos\omega_c t$$

does not have a separate carrier term.


But ... with the help of trigonometric identities and some clever signal processing we may still generate a phase coherent carrier from the received waveform at the receiver.

Let


m(t): zero-mean signal


 $m^2(t)$: non zero-mean signal


and assume

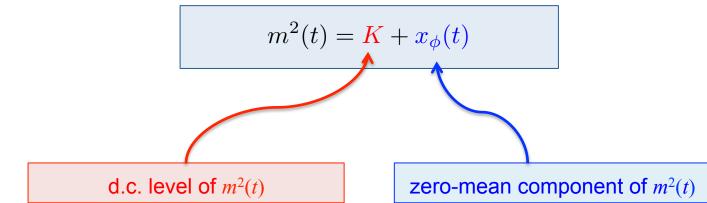

49

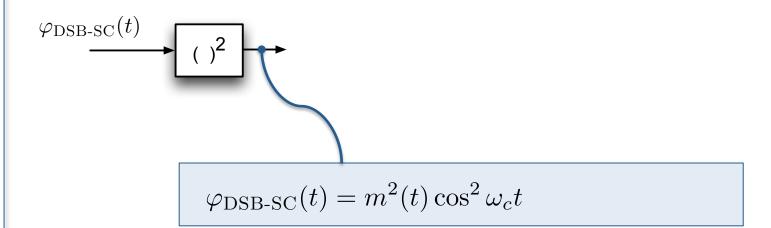

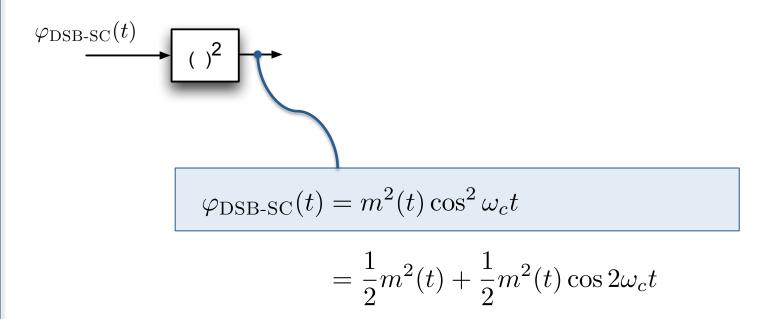


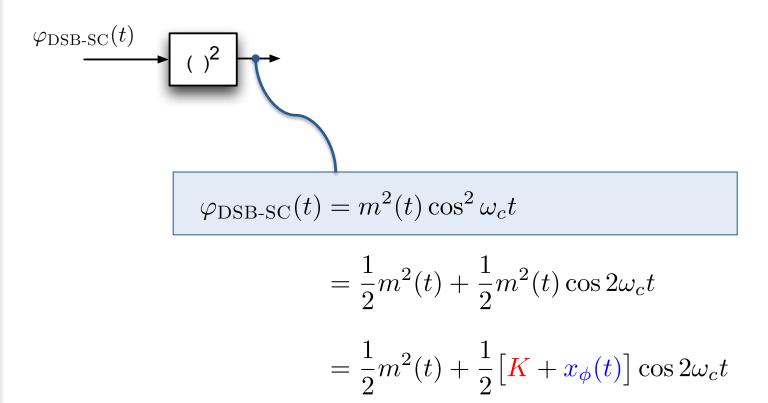

PLL

Analysis

53

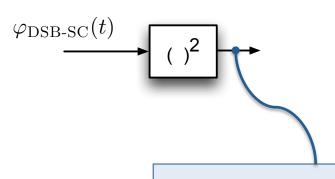


$$\varphi_{\text{DSB-SC}}(t) = m^2(t)\cos^2\omega_c t$$


$$= \frac{1}{2}m^{2}(t) + \frac{1}{2}m^{2}(t)\cos 2\omega_{c}t$$

$$= \frac{1}{2}m^2(t) + \frac{1}{2}\left[\mathbf{K} + x_{\phi}(t)\right]\cos 2\omega_c t$$

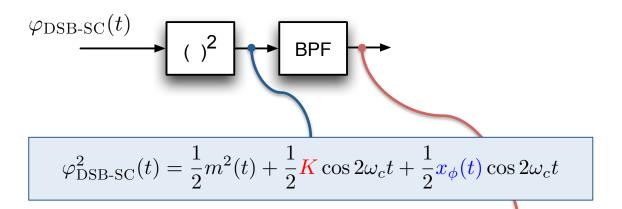
$$= \frac{1}{2}m^2(t) + \frac{1}{2}K\cos 2\omega_c t + \frac{1}{2}x_{\phi}(t)\cos 2\omega_c t$$




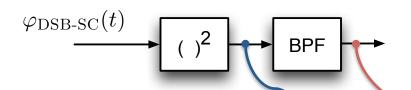
$$\varphi_{\text{DSB-SC}}^2(t) * h_{\text{BPF}}(t) = \left[\frac{1}{2} m^2(t) + \frac{1}{2} \mathbf{K} \cos 2\omega_c t + \frac{1}{2} x_{\phi}(t) \cos 2\omega_c t \right] * h_{\text{BPF}}(t)$$



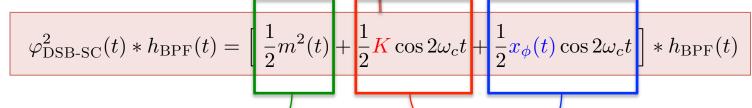
$$\varphi_{\text{DSB-SC}}^2(t) = \frac{1}{2}m^2(t) + \frac{1}{2}K\cos 2\omega_c t + \frac{1}{2}x_{\phi}(t)\cos 2\omega_c t$$




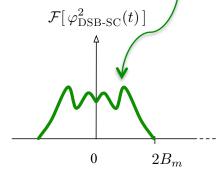

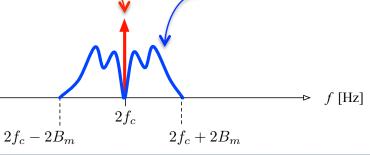

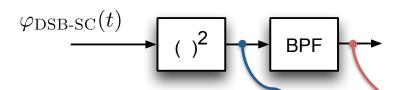
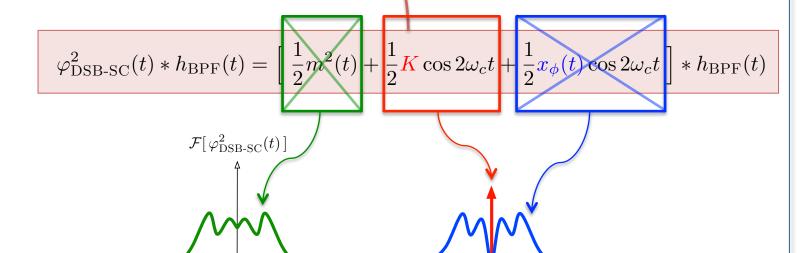
$$\varphi_{\text{DSB-SC}}^2(t) = \frac{1}{2}m^2(t) + \frac{1}{2}K\cos 2\omega_c t + \frac{1}{2}x_{\phi}(t)\cos 2\omega_c t$$



 $2f_c-2B_m$


 $2f_c$

 $2f_c + 2B_m$


 $2B_m$

0

f [Hz]

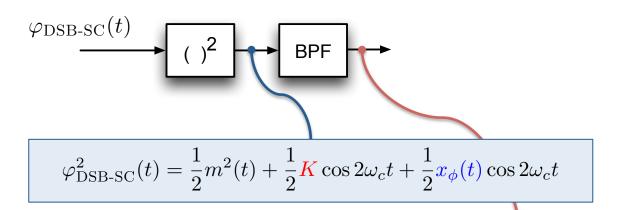

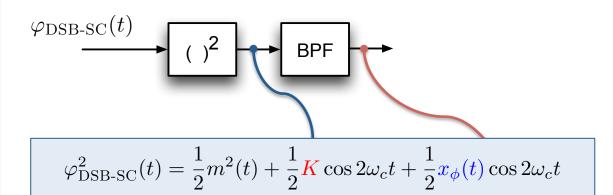
$$\varphi_{\text{DSB-SC}}^2(t) * h_{\text{BPF}}(t) = \left[\frac{1}{2}m^2(t) + \frac{1}{2}K\cos 2\omega_c t + \frac{1}{2}x_{\phi}(t)\cos 2\omega_c t\right] * h_{\text{BPF}}(t)$$



$$\varphi_{\text{DSB-SC}}^2(t) * h_{\text{BPF}}(t) = \left[\frac{1}{2}m^2(t) + \frac{1}{2}K\cos 2\omega_c t + \frac{1}{2}x_{\phi}(t)\cos 2\omega_c t\right] * h_{\text{BPF}}(t)$$


$$= \frac{1}{2}K\cos 2\omega_c t + \left[\text{small residual}\right]$$


$$\approx \frac{1}{2}K\cos 2\omega_c t$$

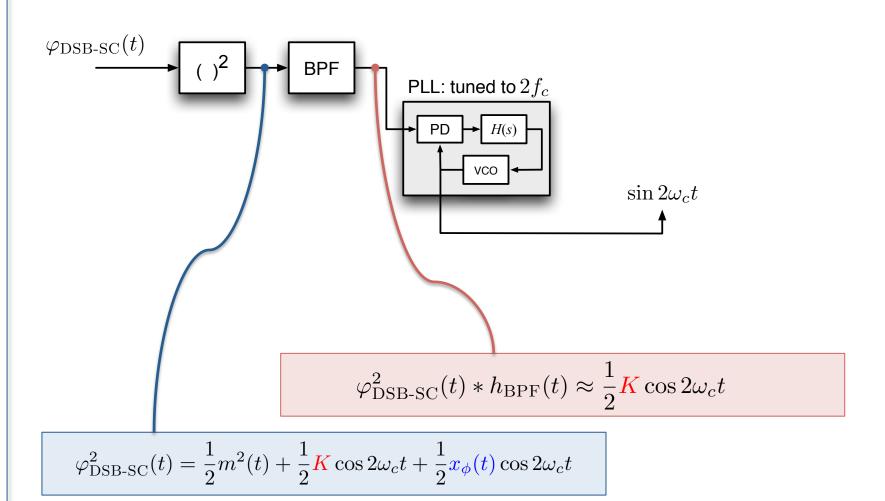

RYERSON UNIVERSITY

ELE 635 - Winter 2015

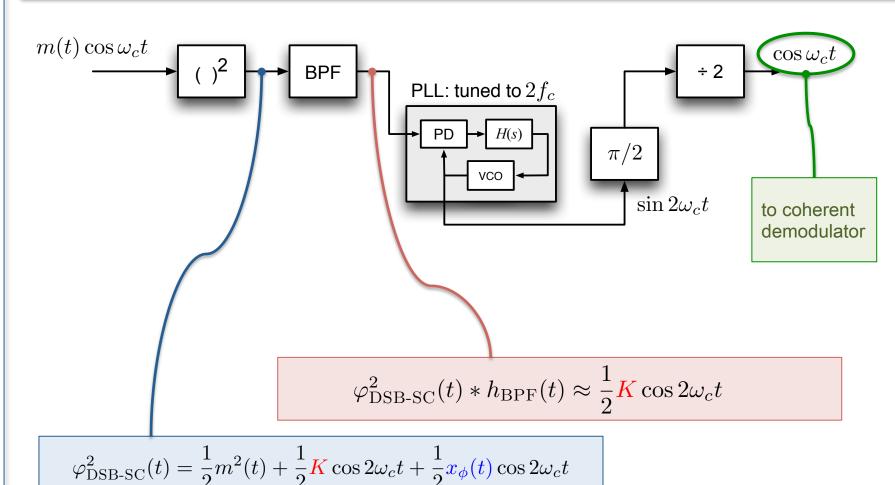

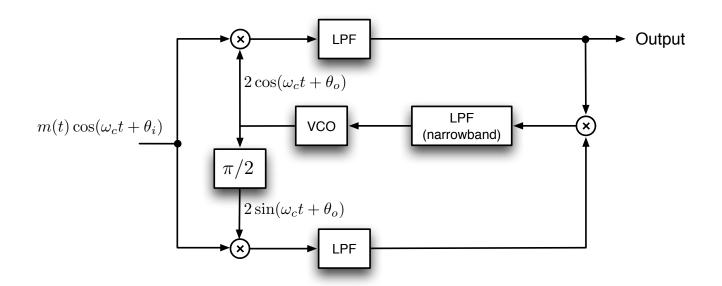


Initialization

PLL


Analysis

- Input: $\varphi_{\text{DSB-SC}}(t) = m(t)\cos(\omega_c t + \theta_i)$
- VCO adjusted to generate a sinusoid at the carrier frequency f_c and with an arbitrary/random phase θ_o : $\cos(\omega_c t + \theta_o)$

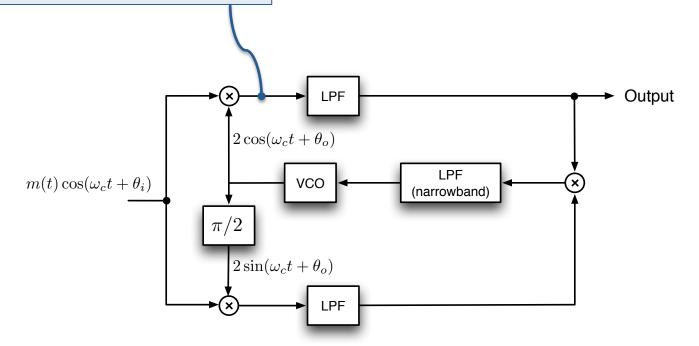
$$2m(t)\cos(\omega_c t + \theta_i)\cos(\omega_c t + \theta_o) = m(t)\cos(\theta_i - \theta_o) + m(t)\cos(2\omega_c t + \theta_i + \theta_o)$$



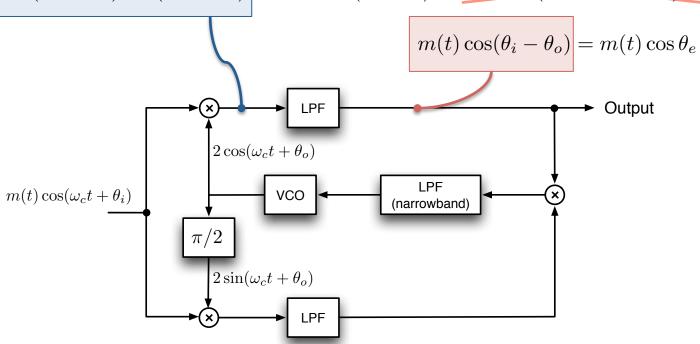
$$2m(t)\cos(\omega_c t + \theta_i)\cos(\omega_c t + \theta_o) = m(t)\cos(\theta_i - \theta_o) + m(t)\cos(2\omega_c t + \theta_i + \theta_o)$$




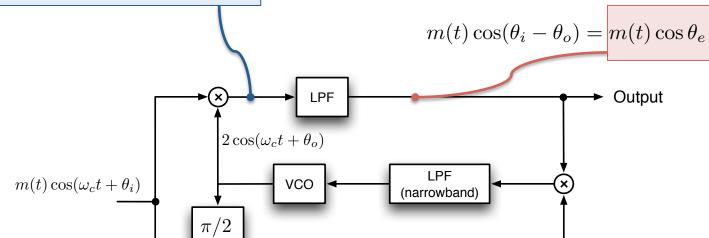
$$2m(t)\cos(\omega_c t + \theta_i)\cos(\omega_c t + \theta_o) = m(t)\cos(\theta_i - \theta_o) + m(t)\cos(2\omega_c t + \theta_i + \theta_o)$$





 $2\sin(\omega_c t + \theta_o)$

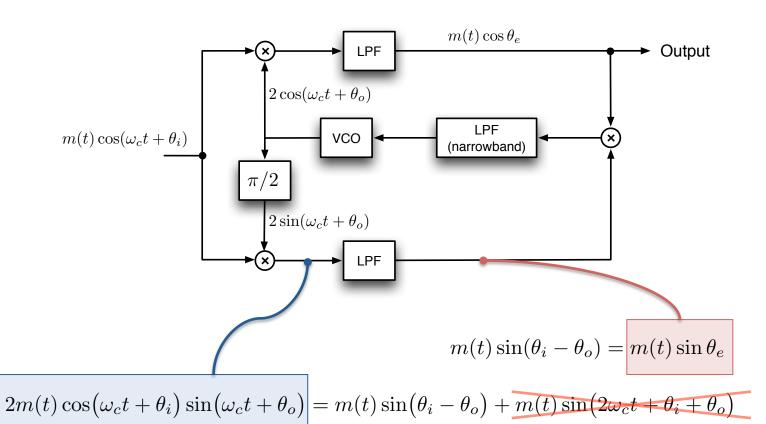


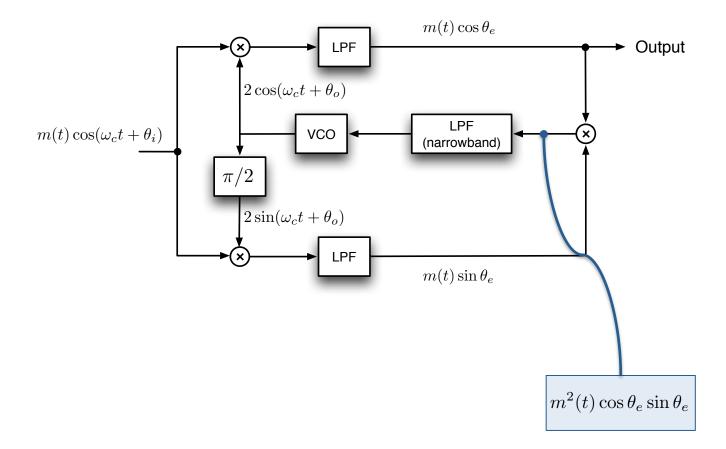

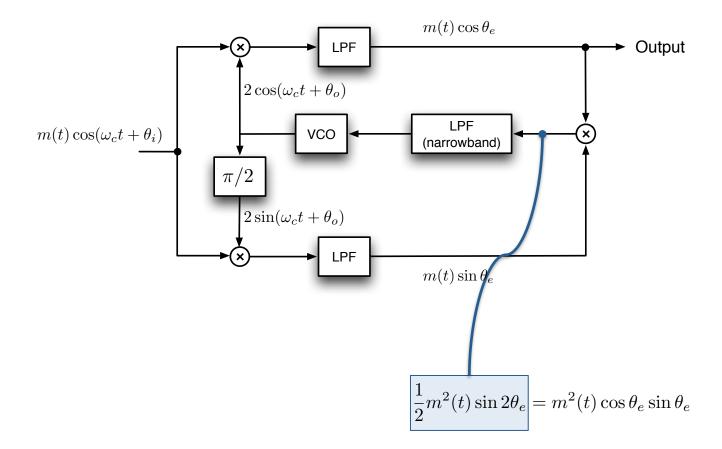


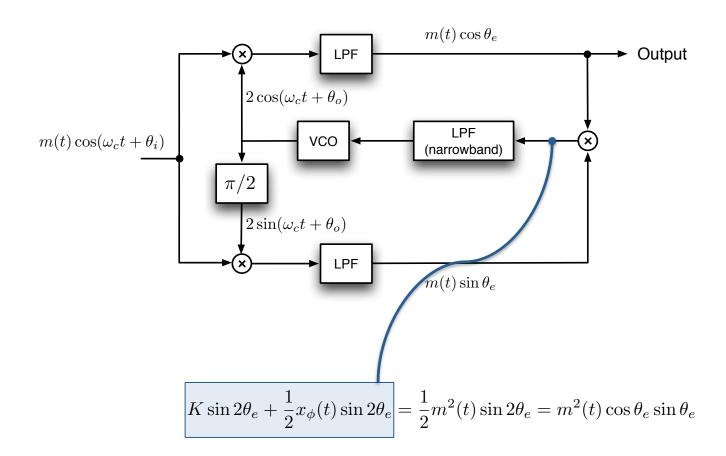

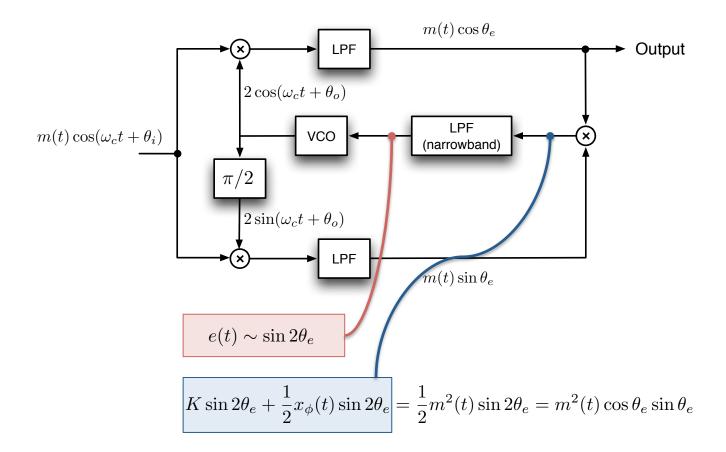


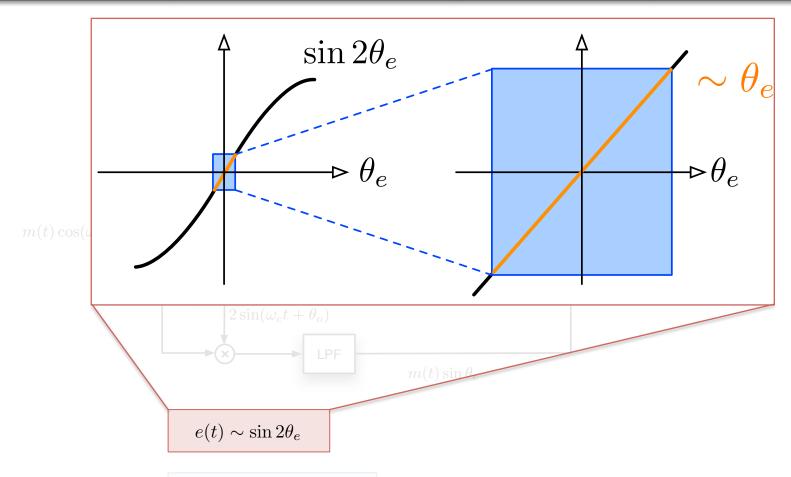


$$\left| K \sin 2\theta_e + \frac{1}{2} x_\phi(t) \sin 2\theta_e \right| = \frac{1}{2} m^2(t) \sin 2\theta_e = m^2(t) \cos \theta_e \sin \theta_e$$

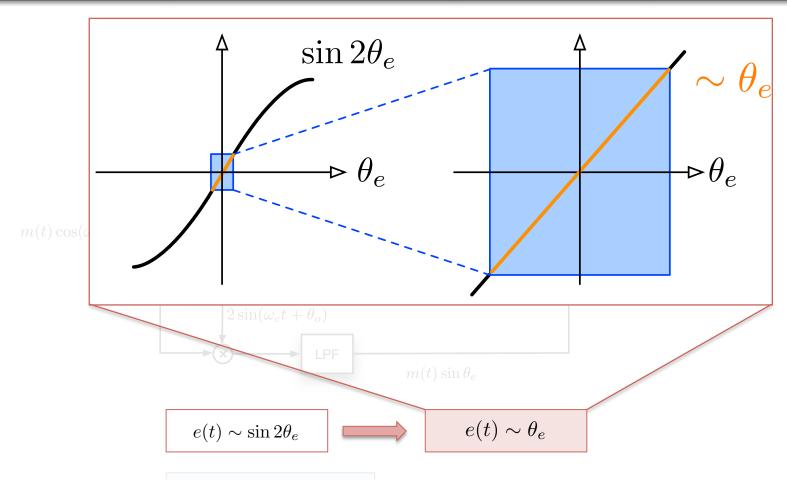

$$\left| K \sin 2\theta_e + \frac{1}{2} x_\phi(t) \sin 2\theta_e \right| = \frac{1}{2} m^2(t) \sin 2\theta_e = m^2(t) \cos \theta_e \sin \theta_e$$

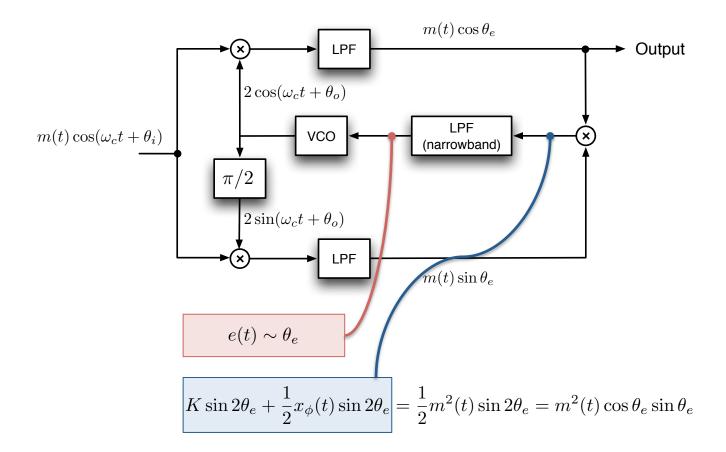

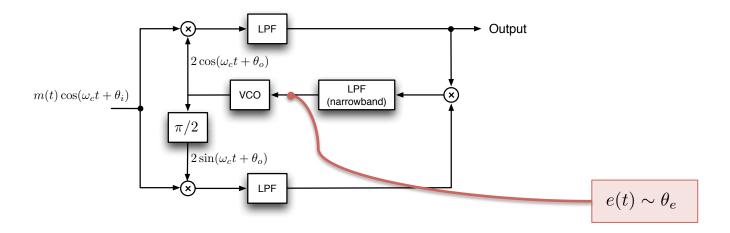

Based on the preceding analysis, we generated a feedback system with:

- VCO input: $e(t) \sim \theta_e = \theta_i \theta_o$
- VCO output: changes to drive the error signal to zero

$$e(t)\longrightarrow 0$$
 \longrightarrow $\theta_o\longrightarrow \theta_i$ phase and frequency coherent carrier